

Laboratory Experiment 6

Including an HVDC Transmission Line for Power Flow Calculations in PowerWorld and Modeling of Thyristor Converters in PSCAD/EMTDC


Objectives:

1. To include an HVDC transmission line and see its effect on power transfer on other transmission line.
2. To understand the operating principle of 12-pulse thyristor converters used in HVDC transmission systems.

Laboratory Tasks and Report:

1. The transmission line between buses 1 and 3 is an HVDC line, as described in the *PowerWorld* file **PowerFlow_HVDCline.pwb** (see video clip# 8), which is located in this Folder. Double click on this file or open it through *PowerWorld*. Look at various characteristics of this HVDC system by examining its parameters; see dialog boxes below. Compare this case with that in Example 5-4 for the various bus voltages and the power flow on various lines due to this HVDC line. Change the set point from 200 MW to 300 MW and then to 400 MW. Explaing what you see.
2. Obtain the waveforms of individual Rectifier DC voltage and combined 12-pulse DC voltage output , for different firing angles , in a 12-pulse thyristor converter operating in a rectifier-mode described by the PSCAD/EMTDC file in this folder called **HVDC_Rectifier.psc** (see video clip# 9). Source: Courtesy of Prof. Ani Golé of the University of Manitoba.
3. Obtain the waveforms of individual inverter DC voltage and combined 12-pulse DC voltage input ,for different firing angles in a 12-pulse thyristor converter operating in the inverter-mode described by the PSCAD/EMTDC file in this folder called **HVDC_Inverter.psc** (see video clip# 9). Source: Courtesy of Prof. Ani Golé of the University of Manitoba.
4. By using the formula (7-12) and (7-13), for different firing angles, calculate the DC voltage and match with the value obtained from the waveform.
For Rectifier: $w \cdot L_s = 13.6791 \text{ ohm}$, $V_{LL} = 213 \text{ kV}$, $I_d =$ Obtain from simulation
For Inverter: $w \cdot L_s = 13.1843 \text{ ohm}$, $V_{LL} = 207 \text{ kV}$, $I_d =$ Obtain from simulation.
5. Obtain the waveforms of the input and output currents for both the transformers in rectifier and inverter. Observe the phase shift between the primary and secondary of Wye-Delta transformer. Explain what you see.
6. Obtain harmonic components of secondary line current of Wye-Delta Transformer and harmonic components of the DC line voltage in the rectifier and inverter. What is the significance of the harmonics that appear?

PowerFlow_HVDCline.pwb

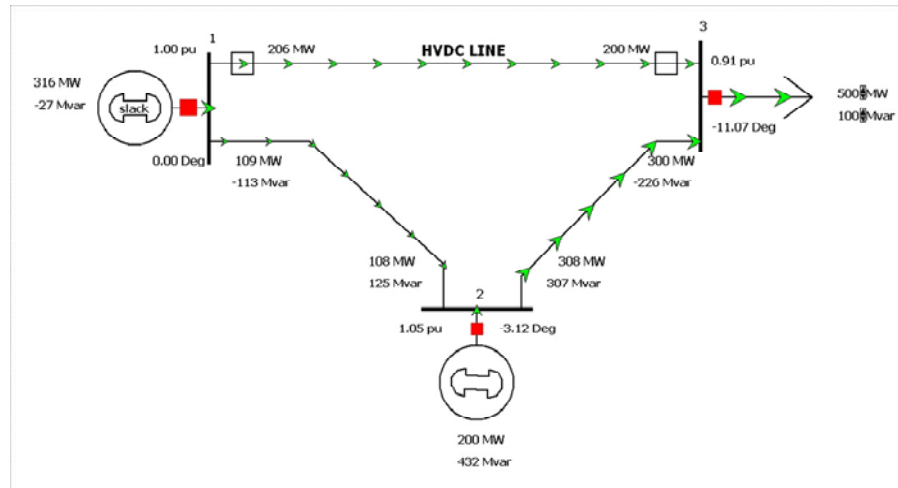

Problem 7-22 HVDC Line between Buses 1 and 3 is set to deliver 200 MW to Bus 3. The voltage at the inverter terminal is 250 kV

DC Transmission Line Options

Line Parameters | Rectifier Parameters | Inverter Parameters | Actual Flow | OPF

	Rectifier Bus	Inverter Bus	Circuit ID
Number	1	3	1
Name	1	3	
Area Name	1	1	

Labels ... no labels

Find By Numbers

Link to New DC Line

Line Parameters

Status

☐ Open

☒ Closed

Control Mode

☐ Blocked

☒ Power

☐ Current

Setpoint

200.0

Resistance

10.000

Sched Voltage

250.0

Switch Voltage

0.0

RComp

0.000

Setpoint Specified at

☐ Rectifier

☒ Inverter

Metered End of Line

☐ Rectifier

☒ Inverter

OK Save Cancel Help

DC Transmission Line Options ✕

Line Parameters
Rectifier Parameters
Inverter Parameters
Actual Flow
OPF

Rectifier

# of Bridges	1	Commutating XF Resistance	0.000
Base Voltage	345.0	Commutating XF Reactance	10.000
XF Ratio	0.6000	Minimum Firing Angle	0.0
XF Tap	1.0000	Maximum Firing Angle	30.0
XF Min Tap	1.0000	Firing Angle	18.1
XF Max Tap	1.0000		
XF Tap Step	0.00625		

✓ OK
Save
✕ Cancel
? Help

DC Transmission Line Options ✕


Line Parameters
Rectifier Parameters
Inverter Parameters
Actual Flow
OPF

Inverter

# of Bridges	1	Commutating XF Resistance	0.000
Base Voltage	345.0	Commutating XF Reactance	10.000
XF Ratio	0.7000	Minimum Firing Angle	5.0
XF Tap	1.0000	Maximum Firing Angle	45.0
XF Min Tap	1.0000	Firing Angle	29.3
XF Max Tap	1.0000		
XF Tap Step	0.00625		

✓ OK
Save
✕ Cancel
? Help

HVDC_Rectifier.psc

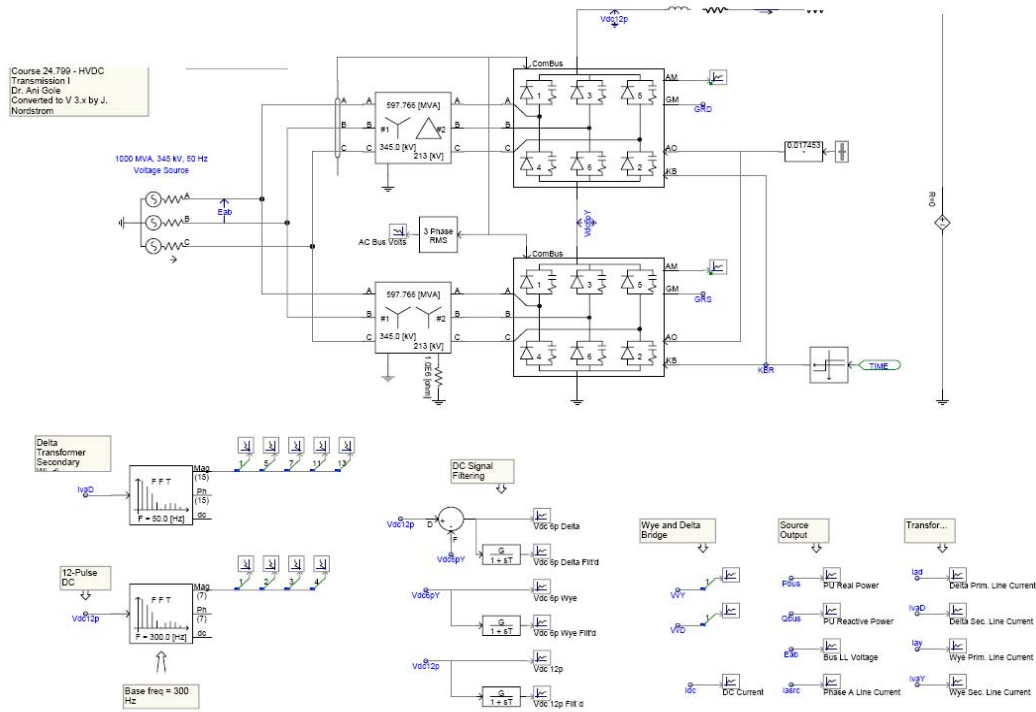

HVDC_Inverter.psc

