

Teaching a Course on
Transformers in Power Systems

Aranya Chakraborty

ECE Department, Texas Tech University,
Lubbock, TX

ONR/EPRI/AEP Faculty Workshop,
Corvallis, OR, July 22, 2009



Existing Power Systems

Course Structure in Texas Tech:

- 15,000 sq. ft laboratory space
- HV Sources, Fast oscilloscopes and digitizers, Advanced electromagnetic field solvers, High speed cameras

- Current research topics:

1. Explosive studies
2. Active rail-gun control
3. Security sensitive weapon development
4. Optimization of semiconductor switching, etc.

- Course structure:


- i. 3 main undergrad course – PP, PE, PS
- ii. 2 main grad courses – PP, PE
- PS (Special topic)

- iii. **This Fall:**

EE 5332 – Power Systems Dynamics and Stability

Spring 2010:


EE 5340 – Power System Identification

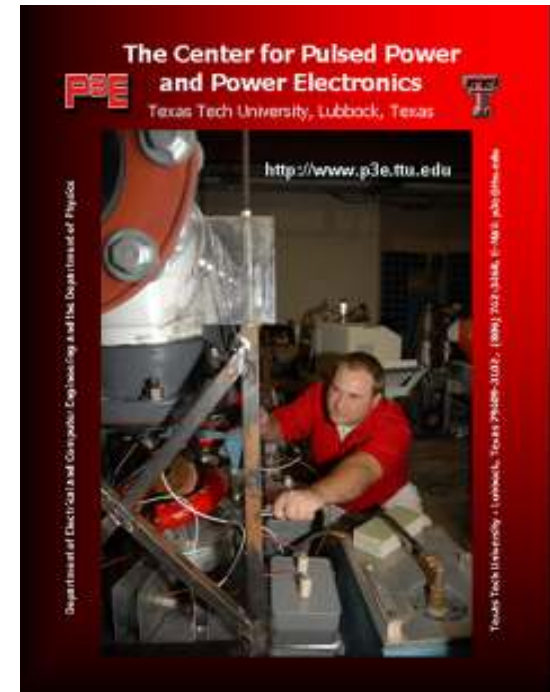

Transformers and Impedance Matching


Definition:

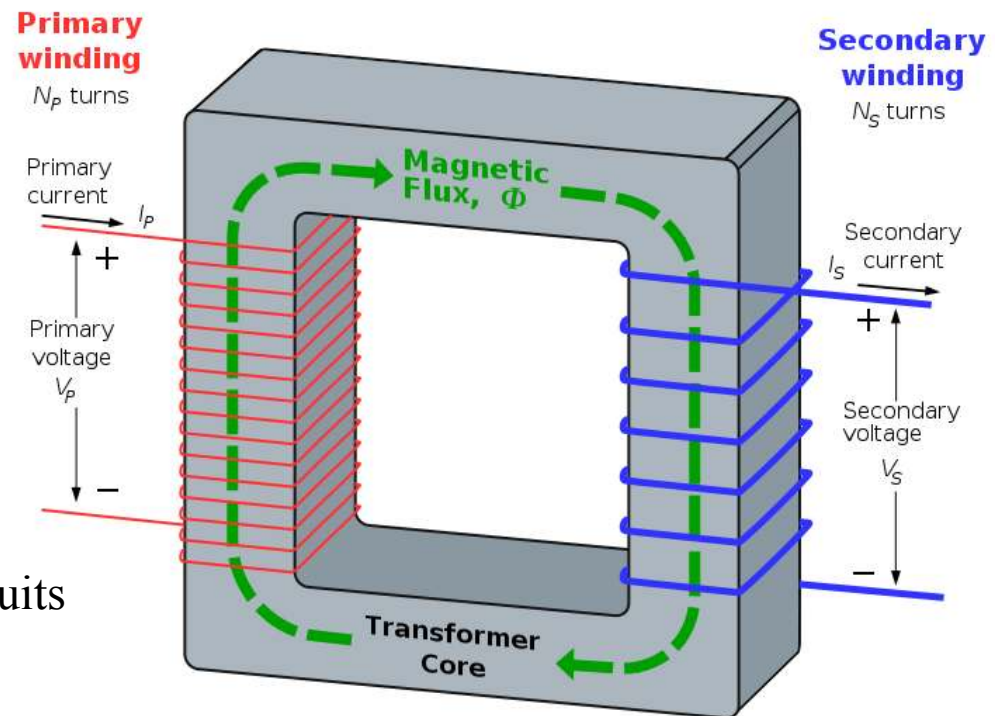- An Electro-magnetic circuit that provides the right voltage for the operation of an electric system
- Can be used to
 - match impedance between circuit & load, two circuits
 - provide isolation
 - match balanced & unbalanced circuits



3 main headings:

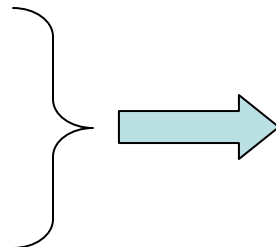- i. Principle of Operation
- ii. Transformer core & geometry
- iii. Types and Applications




All three involve numerical problem solving as well as essay-type (descriptive) questions

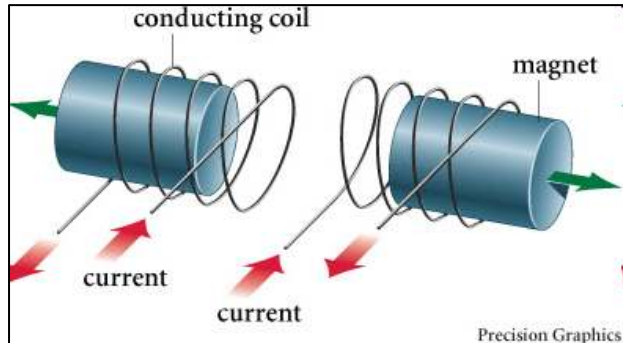
i. Principle of Operation

Principle of Operation

- Faraday's **Law of Electromagnetic Induction**



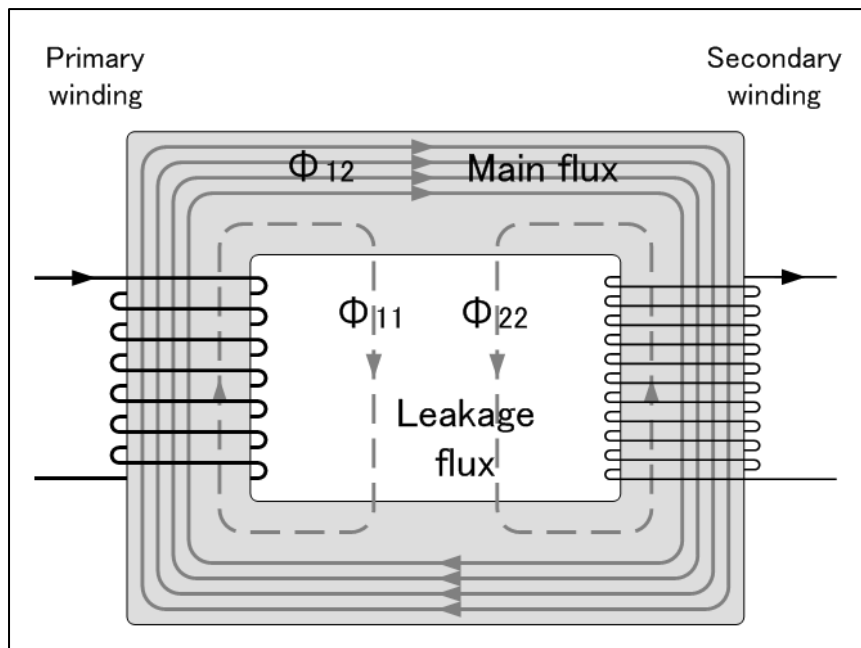When two wires are brought close to each other and one of them carries a fluctuating current, a current will be induced in the other wire.



- The primary and secondary coils are wrapped around an iron **core** of very high **magnetic permeability**.
- Since the same magnetic flux passes through both the **P** and **S** in an ideal transformer,

$$V_p = N_p \frac{d\phi}{dt}, \quad V_s = N_s \frac{d\phi}{dt}$$


$$\Rightarrow \frac{V_p}{V_s} = \frac{N_p}{N_s} \quad \text{Turns ratio}$$

$$\Rightarrow V_p I_p = I_s V_s \quad \text{Power balance}$$

Principle of Operation


- > Students must get familiar with transformer phasor diagrams from the start
- > An excellent way to do this is to teach **No-load** and **On-load** operation in the first few warm-up classes

• No-load

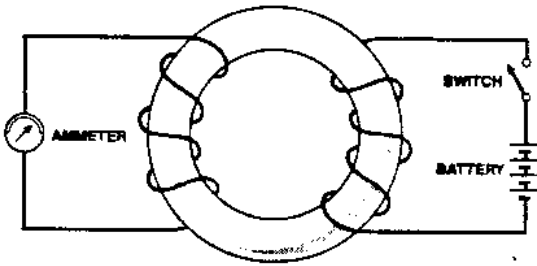

- What is a no-load condition?
- What currents flow through the primary/secondary?
- Are they in phase or out of phase with voltage?
- What is the frequency of the exciting current?
- How does the phasor diagram look like?

• With load

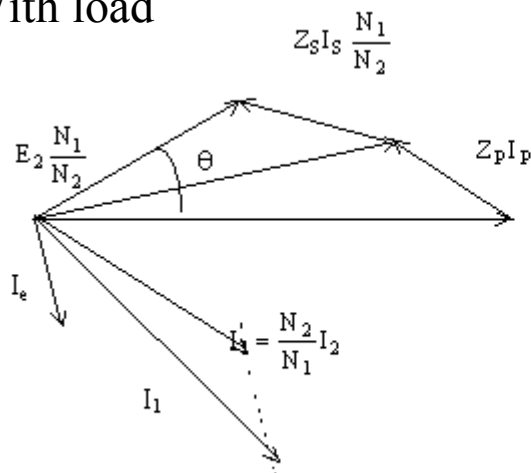


- Extra induction due to secondary current?
- What about current phases/frequency?
- Inductive and Capacitive loads?

I_e = magnetizing current
 I_e = magnetizing current


Next: Magnetic Leakage

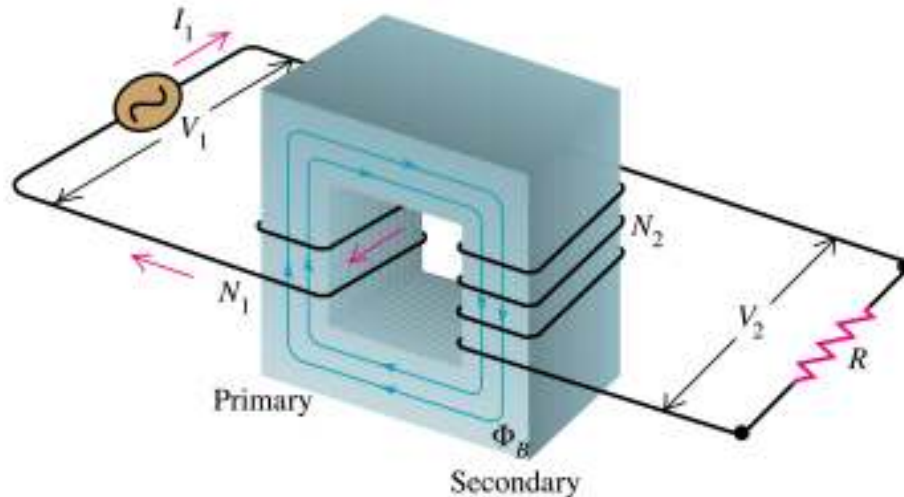How to Interpret a Transformer Electrically?



Copyright © Addison Wesley Longman, Inc.

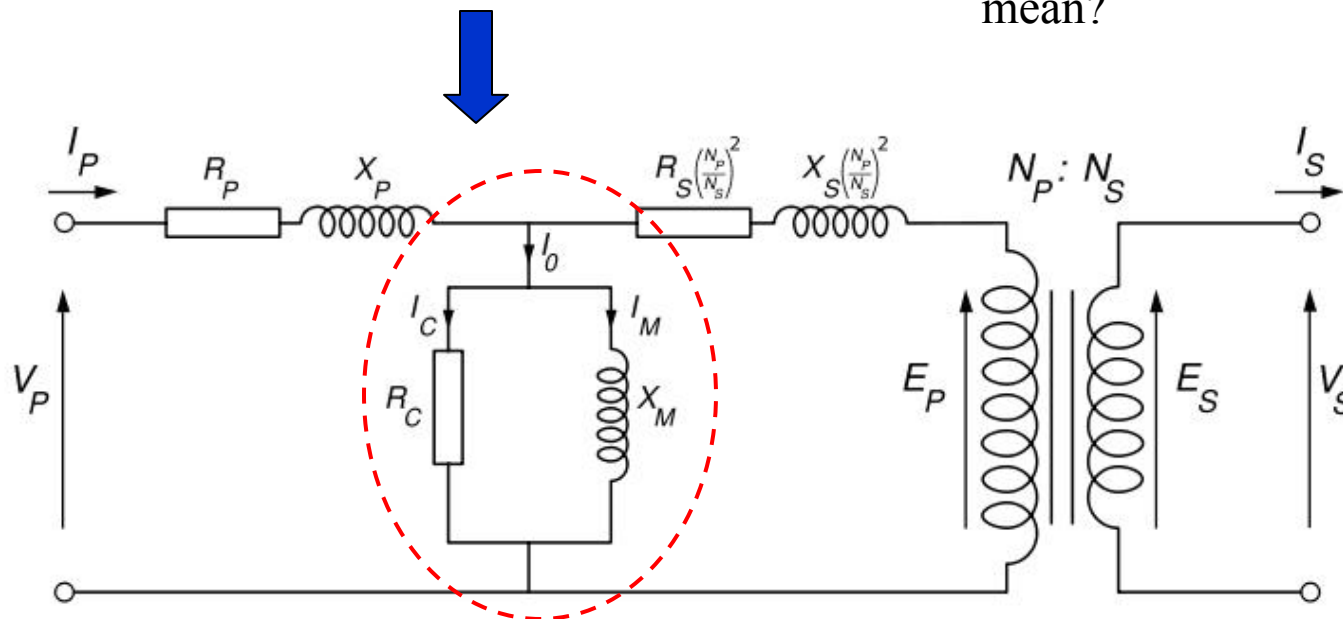- Electrical Engineers look for resistance and reactances, & circuit structure
- Gives them confidence in viewing the physical system mathematically
- What do each resistance and reactance mean?




* Why parallel?

* When can be neglected?

* What effect on operation?

What is the Problem with DC?

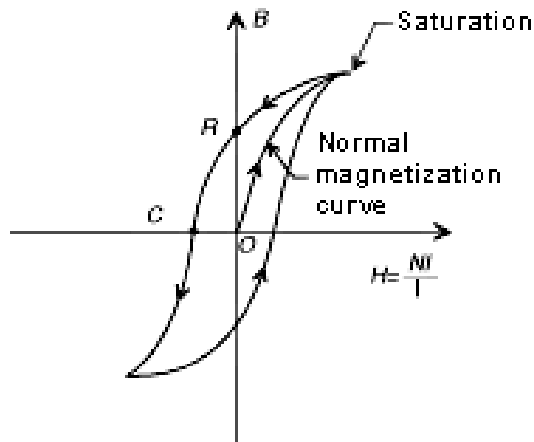

- Hypothetically an ideal transformer would work with direct-current excitation, but



Recall Faraday's Law

$$V_p = N_p \frac{d\phi}{dt} \Rightarrow \phi = \int_0^t \frac{V_p}{N_p} dt = \frac{V}{N_p} t$$



Monotonic increase in flux!

- In practice, the flux would rise to the point where **magnetic saturation** of the core occurs, causing a huge increase in the magnetizing current and overheating the transformer.






AC excitation produces bounded periodic flux, avoiding this problem

- DC Transformer or DC/DC Converter (boost, buck) are realized through power electronic devices

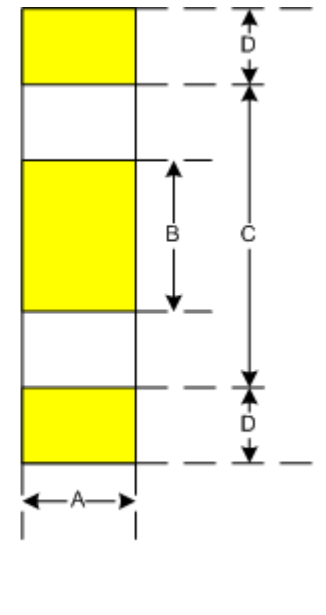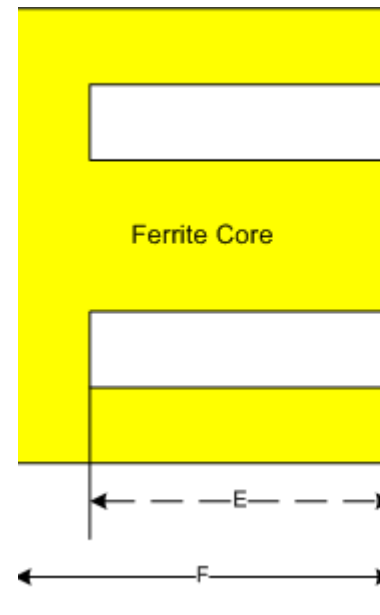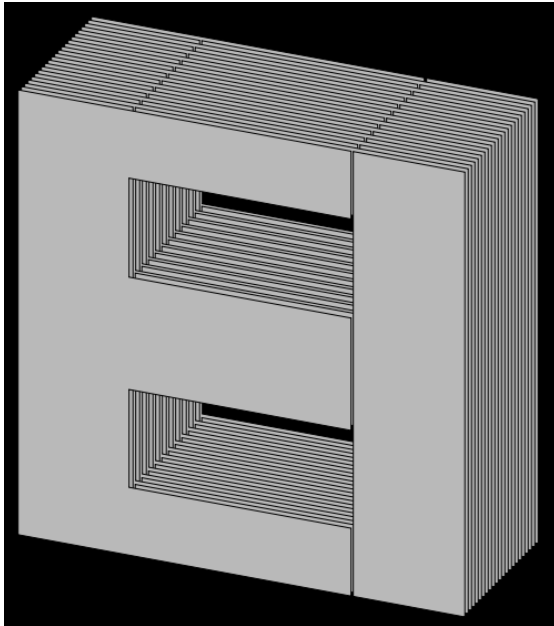ii. Transformer Core and Geometry

Transformer Core & Geometry


- Ferromagnetic core increases the flux coupling far more than air core



- Utility transformers (60 Hz operation) typically use E-core
 - Shell winding (maximum coupling, high efficiency)
 - Core winding (higher voltage)
- Other types – Solenoid core, O-core, Pot core, Toroidal core (higher frequency)



Numerical Problems on T/R Geometry

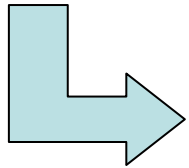

- Optimization of Geometry for enhanced performance
- Detailed dimensioning
- Understanding the importance of each step of design
- **Detailing will take time**



SPICE Software

Can be taught as a *separate computer-oriented design* course
(Ex: Senior capstone project)

Main Steps:


1. Determine core size
2. Evaluate peak flux density
3. Compute turn ratio
4. Compute coil size, losses
5. **Iterate!**



Magnetizing current below given value?



Transformer Losses & Efficiency

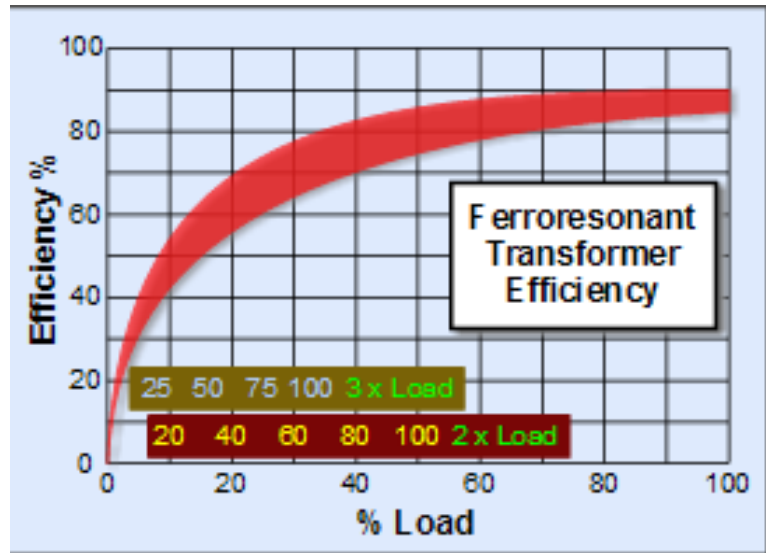

Losses:


1. Core loss/Iron loss
 - includes hysteresis and Eddy current loss
 - practically same for all loads
2. Copper loss:
 - due to resistance in windings
 - proportional to current square

Efficiency = 1 – loss/input → loss is in VA, input is in Watts,
so efficiency is dependent on power factor

$$= 1 - \frac{x / \cos \phi}{1 + x / \cos \phi} \quad (\phi = \text{secondary pf}, x = V_2 I_2 / \text{loss})$$


• Condition for Maximum Efficiency:

→ **Copper loss = Iron loss**

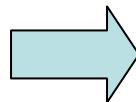

An effective way for students to evaluate
their individual designs

All-day Efficiency

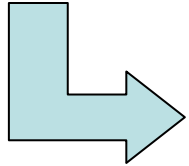

Transformer design is an excellent chance to learn about **All-day efficiency**



$$\eta_{ad} = \frac{\text{output in } KWh}{\text{input in } KWh} \quad (\text{for 24 hours})$$

- Distribution transformers supply no load at night
- • **Only core loss, very little copper loss**
- All-day efficiency captures this effect based on the extent the t/r is **used** in a day

Numerical Example:

500 KVA t/r, Cu loss=4.5KW, Fe loss=35. KW at full load. Daily loading is:

- 400 KW (0.8 pf) for 6 hours
- 300 KW (0.75 pf) for 10 hours
- 100 KW (0.8 pf) for 4 hours
- 4 hours of no load



} **Calculate ADE**

iii. Transformer Types and Applications in Power Systems



Transformer Types & Applications

1. Power Transformers
2. Distribution Transformers
3. Isolation Transformers
4. Auto-transformers

Power Transformer

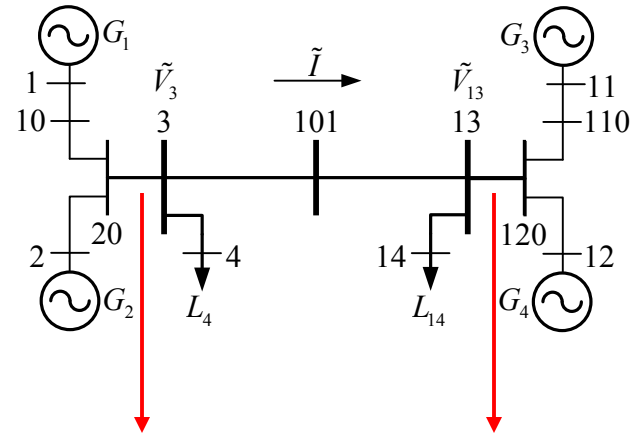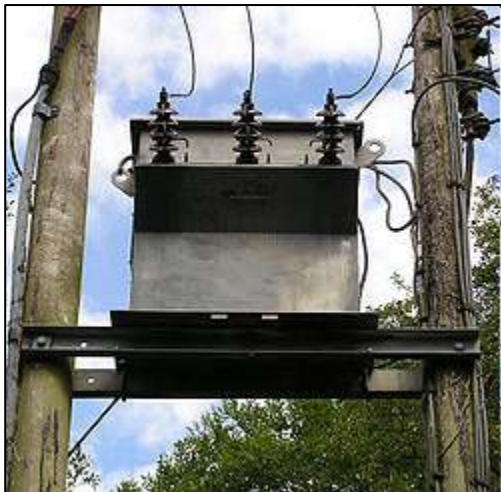

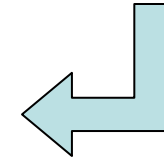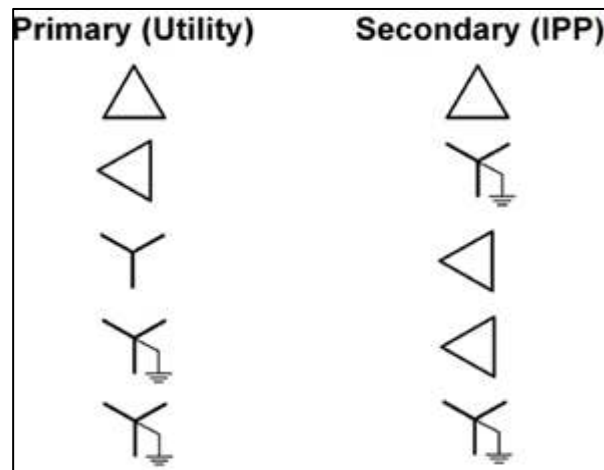
- High voltage transmission to reduce I^2R losses
- Must have heavy windings to withstand $P=EI$
- If load increases excessively then circuit breakers open for transformer protection



3-phase connection
is important

3-phase Transformer Connections

Three-phase transformer core



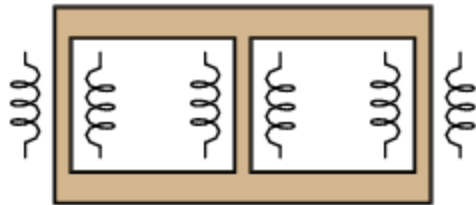


Primary - Secondary

Y	-	Y
Y	-	Δ
Δ	-	Y
Δ	-	Δ


- 3-ph t/r core has three sets of windings.
- P & S windings will be connected in either Δ or Y configurations
- Y connections provide the opportunity for multiple voltages
- Δ connections enjoy a higher level of reliability (if one winding fails open, the other two can still maintain full line voltages to the load).

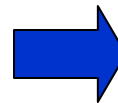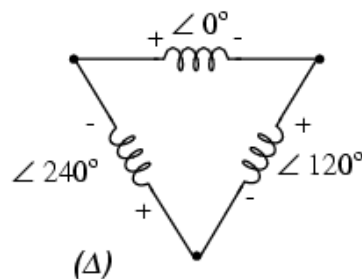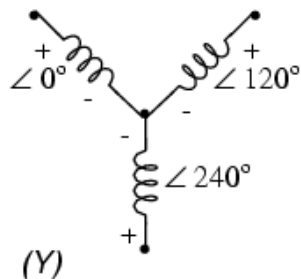Extremely Important – Proper Winding Phasing:



- Y: The center must tie all “-” or “+”
- Δ : The winding polarities must stack in a complementary manner (+ to -).


3-phase Transformer Connections

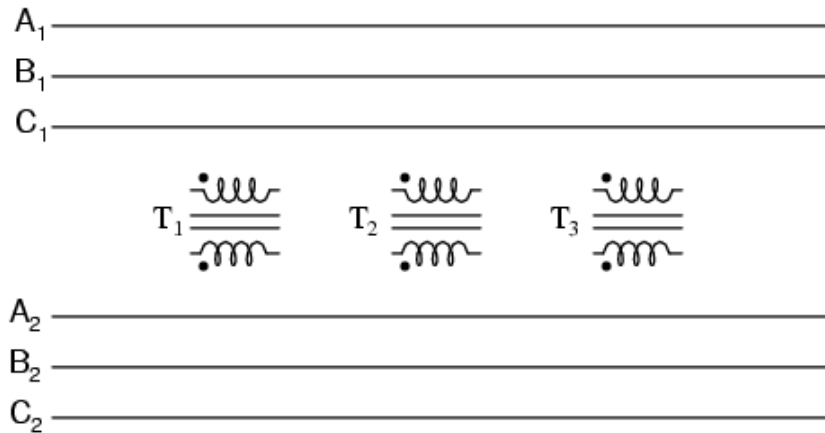



Computer software may be used for complex multiple winding connections



Y - Y

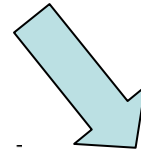


Y - Δ

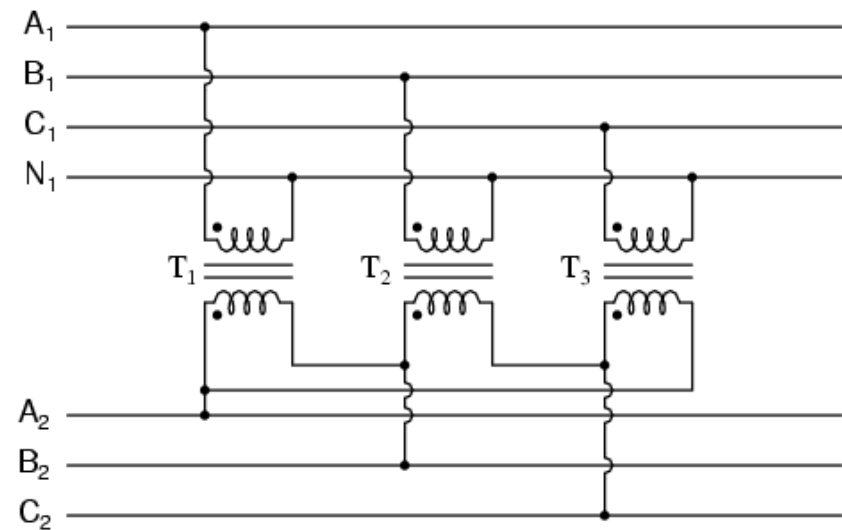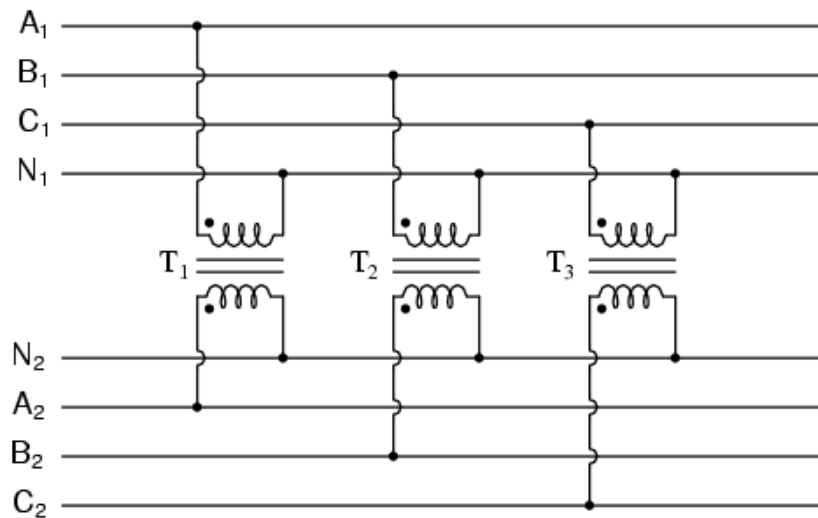


What Happens with Wrong Winding?

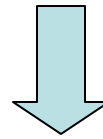- Students must understand the effect of wrong winding connections
- Catastrophic? Harmful? Brownout?





Not really!

Take a single-phase example:

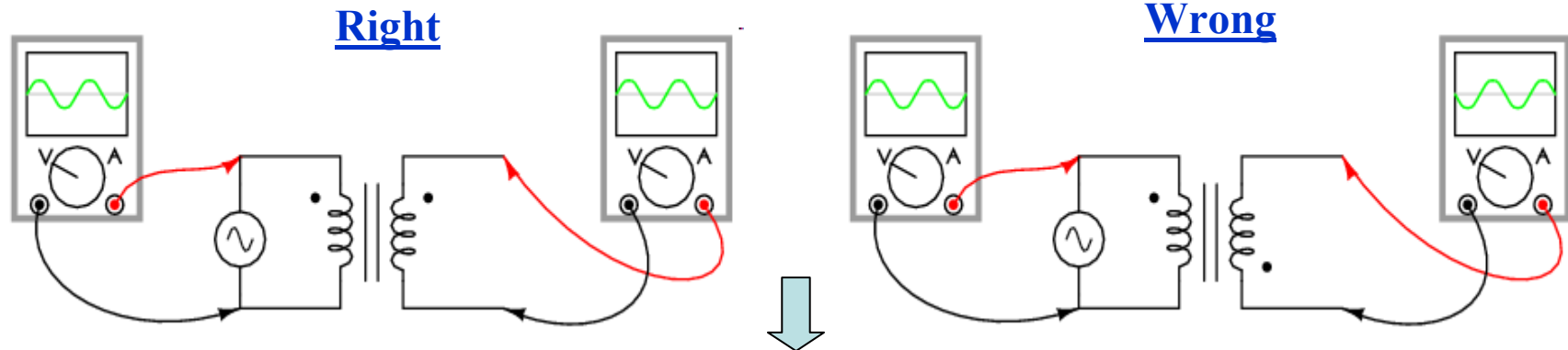

Look at the oscilloscopes: Phase reverses by 180 deg

Changing it is easy
as well

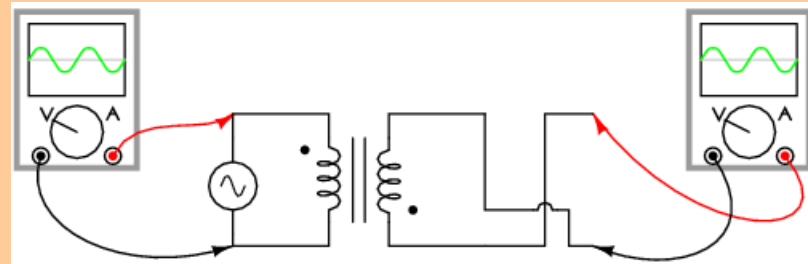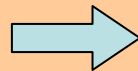


Distribution Transformer

- Converts higher voltage (usually 11-22-33kV) to a lower voltage (250 or 433V) with same frequency
- Pole-mounted, ground-mounted, integrated transformer substation

Isolation Transformer

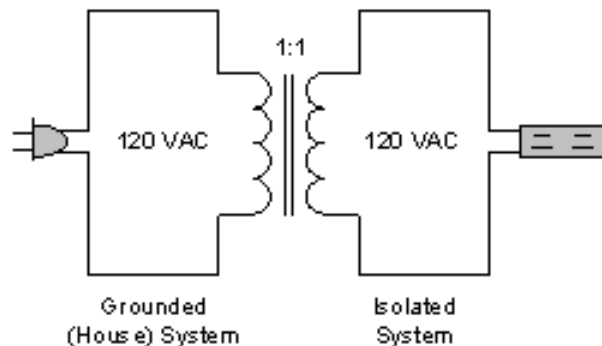
- Capacitance from a winding to any nearby conductor - such as other windings, the core, and the chassis
- This capacitive coupling mechanism can carry high frequency noise on the input primary to the output secondary windings or vice versa.
- Isolation transformers are designed to minimize this coupling



Turn ratio 1:1 as no voltage boost/buck is required

Auto-Transformer



Autotransformer

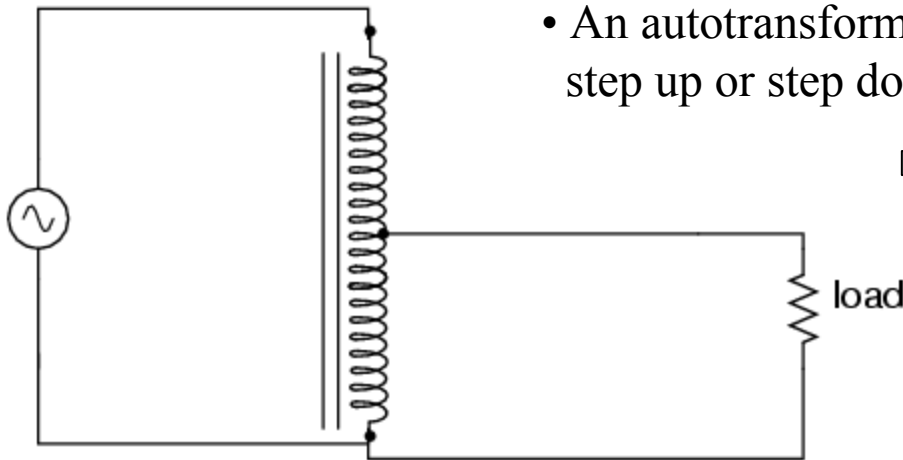

- An autotransformer is a **single**, tapped inductor coil used to step up or step down voltage like a transformer (cheap)

➡ No electrical isolation, however.

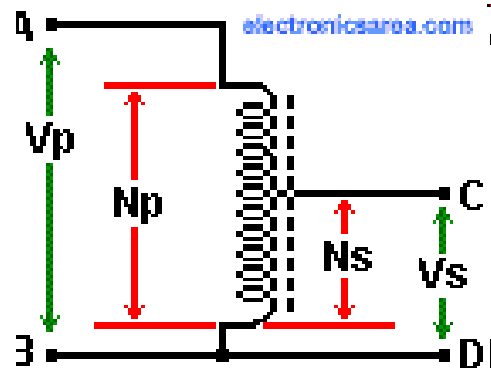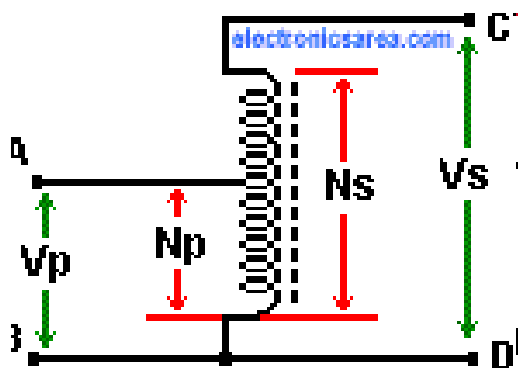
Main points: 1. Operation
2. Phasor Diagram
3. Pros, Cons



Boosting and **Bucking**
totally depend on **taps**

- Applications: On long rural power distribution lines, special autotransformers with automatic tap-changing equipment are inserted as **voltage regulators (VARIAC)**₂₀

Transformer Tests

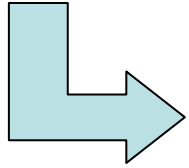

Laboratory tests have to be set up so that students can compute the equivalent circuit of a real transformer



- Open circuit test: to determine no-load iron loss



Hysteresis: *Steinmetz's* empirical relation

Eddy current: square of frequency

$$W_{iron} = W_h + W_e = PB_{max}^{1.6} f^2 + QB_{max}^2 f^2$$

- Short circuit test: to determine leakage reactance, equivalent impedance, copper loss, voltage regulation

→ Lab sessions must be integrated with group projects for calculations

→ Can be a part of design project as well

Interesting Class Project Problems

Topic # 1: Phase Shift Control

- Transformers can be used for phase shifting between two generators to vary active power flow in a line
- Direct PST's phase shift is obtained by connecting the windings appropriately.


$$P = \frac{E_1 E_2}{x_e} \sin(\delta + \alpha)$$

→ **Some interesting things students can explore:**

- * Different connections and different resulting
- * How does the power angle curve change?
- * Any effect on voltage amplitude?
- * Does this affect the PV curve?

Topic # 2: Load Balancing

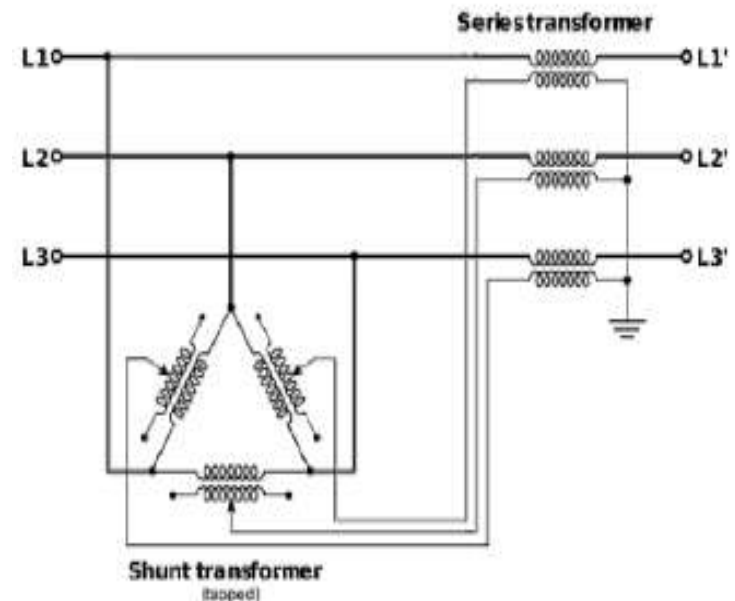Topic # 3: Voltage Optimization & Regulation




Conclusions

- By the end of the course, students should understand:



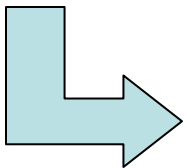- ➡ Transformers: what and why
- ➡ Equivalent circuit, vector diagrams
- ➡ Loss, Efficiency, how to calculate them?
- ➡ 3-ph connection, phase shift, variac



- * Study of transformers is important, but is tough and dry
- * Visual aids can be helpful – **pictures, phasors, graphics**
- * Interesting projects can be useful as well
- * Should not be restricted to dry mathematics
- * Practical lab tests are **essential**