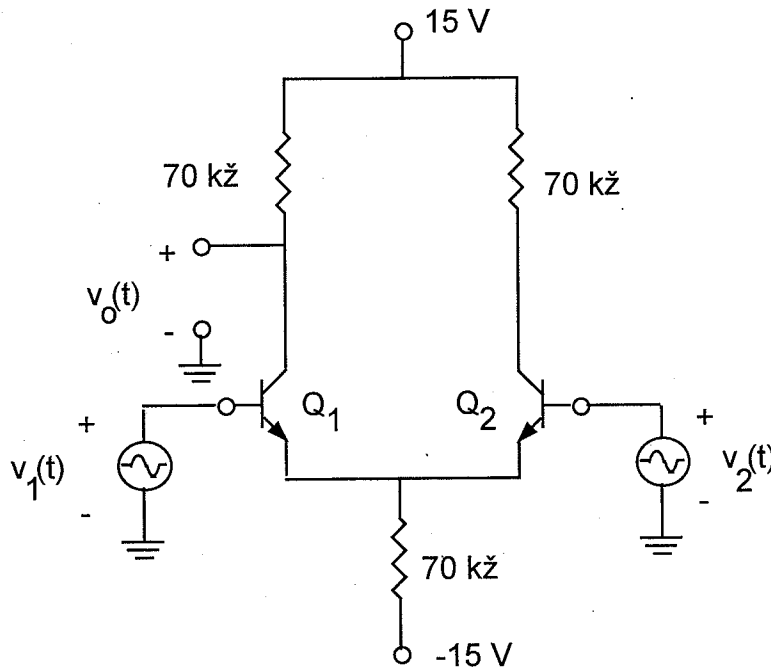


Electronics Problem – Fall 2006 ECE Qualifying Exam


Consider the amplifier shown below. The BJT characteristics are also given.



Silicon BJT	
Beta =	100
Early Voltage =	100 V
f_T =	100 MHz
C_π =	3 pF
C_μ =	2 pF

1. Determine the voltage gain $\frac{v_o}{(v_1 - v_2)}$.
2. Determine the common mode rejection ratio.
3. Add negative feedback to the amplifier to produce a closed-loop amplifier with a single-ended input (ground-referenced input) having an input resistance of 1 MΩ. Show the feedback circuit on the amplifier circuit diagram including values of the feedback circuit elements.
4. What is closed-loop voltage gain of the amplifier?

①

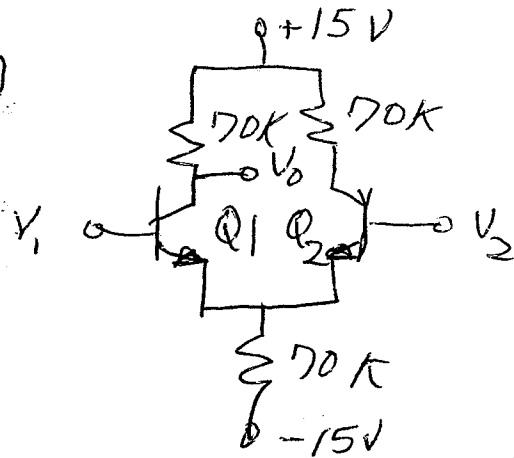

$$I_{C1} = \frac{(15 - 0.7)}{70k} \times \frac{1}{2}$$

$$I_{C1} \approx 0.1mA$$

$$\frac{v_o}{(v_1 - v_2)} = \frac{g_m R_c}{2}$$


$$g_m = \frac{0.1mA}{0.025V} = 4 \times 10^{-3} \text{ S}$$

$$\frac{v_o}{v_1 - v_2} = \frac{(4 \times 10^{-3})(7 \times 10^4)}{2} = \boxed{140}$$

②

$$CMRR = \frac{R_E}{2R_c} \sim \frac{70k}{(2)(70k)} \sim \frac{1}{2}$$

③

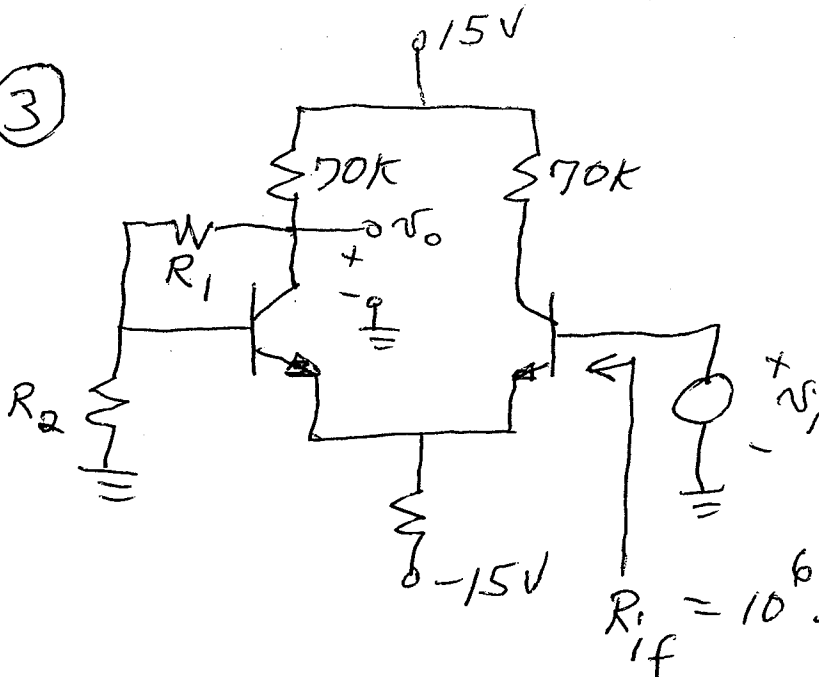

Assume R_1, R_2 feedback ckt does not load open-loop amplifier

$$R_1 + R_2 \gg 70k$$

$$R_{if} = 10^6 \Omega = R_i (1 + A_o B)$$

$$R_i = \text{open-loop amp. input impedance} = 2r_{\pi}$$

Fall 2006

$$r_{\pi} = \frac{25 \times 10^{-2} \text{ V}}{(10^{-4} \text{ A}) / (100)} = 25 \text{ k}\Omega; R_i = 50 \text{ k}\Omega$$

SOLUTION - Electronics

Pg. 2 of 2

$$10^6 = 5 \times 10^4 (1 + A_o \beta)$$

$$A_o \beta + 1 = 20$$

$$A_o \beta = 19; A_o = 140$$

$$\beta = \frac{19}{140} \approx 0.14 = \frac{R_2}{(R_1 + R_2)}$$

$$0.14 R_1 + 0.14 R_2 = R_2$$

$$R_1 = \frac{0.86}{0.14} R_2 = 6.14 R_2$$

$$\text{Set } R_1 + R_2 = 10^6 \Omega$$

$$6.14 R_2 + R_2 = 10^6$$

$$R_2 = \frac{10^6}{7.14} = 140 \text{ k}\Omega = R_2; R_1 = 860 \text{ k}\Omega$$

$$\textcircled{4} A_f = \frac{140}{1+19} = 7 = A_f$$