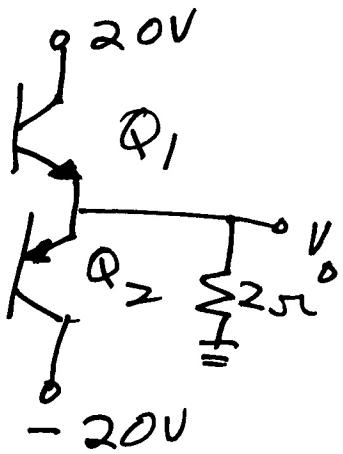


Problem #4 Solutions: Electronics

2013 PhD Qualifying Exam

- ① Maximum instantaneous C-E voltage = 40V.



Q₁ Near cutoff

Q₂ Near saturation

$$V_{CE1} = V_{C1} - V_{E1}$$

$$+20V - 20V$$

With 50% factor of safety

$$\boxed{\text{Voltage rating} \geq 40(1.5) = 60V}$$

- ② $I_{C,\max} = \frac{20V}{25\Omega} = 10A = \text{max instantaneous collector current.}$

With 50% factor of safety

$$\boxed{I_{C,\max} \geq (10)(1.5) = 15A}$$

- ③ $\langle P_c \rangle = \frac{\langle P_{cc} \rangle - \langle P_L \rangle}{2} = \text{average power dissipated in a BJT}$

$\langle P_{cc} \rangle$ = average power provided by
20 V supplies

$$P_{cc}(t) = V_{cc} I_c(t) \quad 0 < t < T/4$$

$$I_c(t) = \frac{V_p}{R_L} \left[\frac{t}{T/4} \right]$$

$$\langle P_{cc} \rangle = \frac{4}{T} \int_0^{T/4} \frac{V_{cc} V_p}{R_L} \frac{4}{T} t dt = \frac{V_{cc} V_p}{2 R_L}$$

$\langle P_L \rangle$ = average power dissipated in R_L

$$P_L(t) = \left\{ \frac{V_p t}{\frac{T/4}{R_L}} \right\}^2 \frac{1}{R_L} \quad 0 < t < \frac{T}{4}$$

$$\langle P_L \rangle = \frac{4}{T} \int_0^{T/4} \frac{V_p^2}{(\frac{T/4}{R_L})^2} t^2 dt = \frac{V_p^2}{3 R_L}$$

$$2 \langle P_c \rangle = \frac{V_{cc} V_p}{2 R_L} - \frac{V_p^2}{3 R_L}$$

$$2 \frac{d \langle P_c \rangle}{d V_p} = 0 = \frac{V_{cc}}{2} - \frac{2}{3} V_p ; \quad V_p = \frac{3 V_{cc}}{4}$$

$$\langle P_c \rangle_{\max} = \frac{1}{2} \left\{ \frac{V_{cc}}{2 R_L} \times \frac{3 V_{cc}}{4} - \frac{1}{3 R_L} \left(\frac{3 V_{cc}}{4} \right)^2 \right\}$$

$$\langle P_c \rangle_{\max} = \frac{3V_{CC}^2}{16R_L} - \frac{9V_{CC}^2}{96R_L}$$

$$\langle P_c \rangle_{\max} = \frac{3V_{CC}^2}{16R_L} \left(1 - \frac{3}{6}\right) = \frac{3V_{CC}^2}{32R_L}$$

Put in numbers

$$\langle P_c \rangle_{\max} = \frac{3}{32} \frac{(20)^2}{2} = \frac{1200}{64} = \boxed{18.75W}$$

④ At max signal swing $V_p = V_{CC}$

$$\langle P_{CC} \rangle = \frac{(20)^2}{(2)(2)} = \frac{400}{4} = 100W$$

$$\langle P_L \rangle = \frac{(20)^2}{(3)(2)} = \frac{400}{6} = 66.7W$$

$$\eta_{\max} = \frac{66.7}{100} = 66.7\%$$

$$T_{J,\max} = \langle P_c \rangle_{\max} R_{\theta,ja} + 35^\circ C$$

$$= (18.75)(5) + 35 = 94 + 35$$

$$T_{J,\max} = 129^\circ C$$