

This problem tests your knowledge of synthesizing combination and sequential logic, state machines, and switching circuits.

1. **Representations of Boolean Functions** [1.0 points]

For the function defined by the following truth table:

$a$	$b$	$c$	$d$	$f(a, b, c, d)$
0	0	0	0	0
0	0	0	1	1
0	0	1	0	1
0	0	1	1	1
0	1	0	0	0
0	1	0	1	0
0	1	1	0	0
0	1	1	1	0
1	0	0	0	1
1	0	0	1	0
1	0	1	0	1
1	0	1	1	1
1	1	0	0	0
1	1	0	1	1
1	1	1	0	1
1	1	1	1	1

- Give the Boolean expression corresponding to a minimal two-level AND-OR circuit (i.e., AND gates in the first level and an OR gate in the second level).
- Give the Boolean expression corresponding to a minimal two-level OR-NAND circuit (i.e., OR gates in the first level and a NAND gate in the second level).
- Give the Boolean expression corresponding to minimal two-level OR-AND circuit (i.e., OR gates in the first level and an AND gate in the second level).
- Give the Boolean expression corresponding to minimal two-level AND-NOR circuit (i.e., AND gates in the first level and a NOR gate in the second level).
- Given the Boolean expression corresponding to a minimal two-level AND-XOR circuit (i.e., AND gates in the first level and an exclusive-OR gate in the second level). Do *not* negate any of the variables in this representation.

2. **State Tables and Graphs** [1.0 points]

A sequential circuit has two inputs ( $X_1, X_2$ ) and one output ( $Z$ ). The output remains a constant value unless one of the following input sequences occurs:

- The input sequence  $X_1, X_2 = 01, 11$  causes the output to become 0.
- The input sequence  $X_1, X_2 = 10, 11$  causes the output to become 1.
- The input sequence  $X_1, X_2 = 10, 01$  causes the output to change value.

Assume that this is a Moore machine. Provide a state transition table and state graph for this circuit.

3. **Flip-Flop Input Equations** [1.0 points]

Consider the following state table for a sequential circuit with input  $X$  and output  $Z$ .

state	next state		$Z$	
	$X = 0$	$X = 1$	$X = 0$	$X = 1$
$S_0$	$S_1$	$S_2$	0	0
$S_1$	$S_3$	$S_2$	0	0
$S_2$	$S_1$	$S_4$	0	0
$S_3$	$S_5$	$S_2$	0	0
$S_4$	$S_1$	$S_6$	0	0
$S_5$	$S_5$	$S_2$	1	0
$S_6$	$S_1$	$S_6$	0	1

Derive flip-flop input equations for an implementation of the circuit with:

- (a) D flip-flops
- (b) J-K flip-flops

4. **Switching Circuit** [1.0 points]

For the switching circuit in Figure 1, write the Boolean function implemented between  $S$  and  $D$ . Each switch is closed if the corresponding variable is 1 and open if it 0. The function evaluates to 1 if there is a closed path from  $S$  to  $D$  and 0 otherwise.

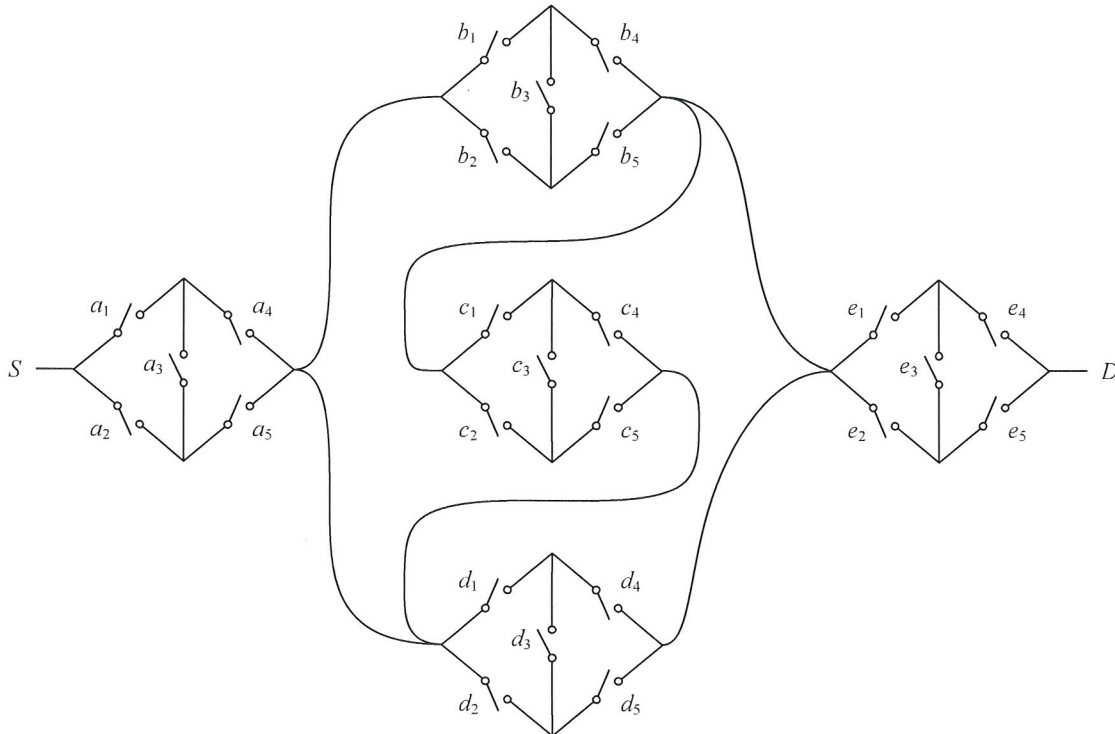


Figure 1: A switching circuit.