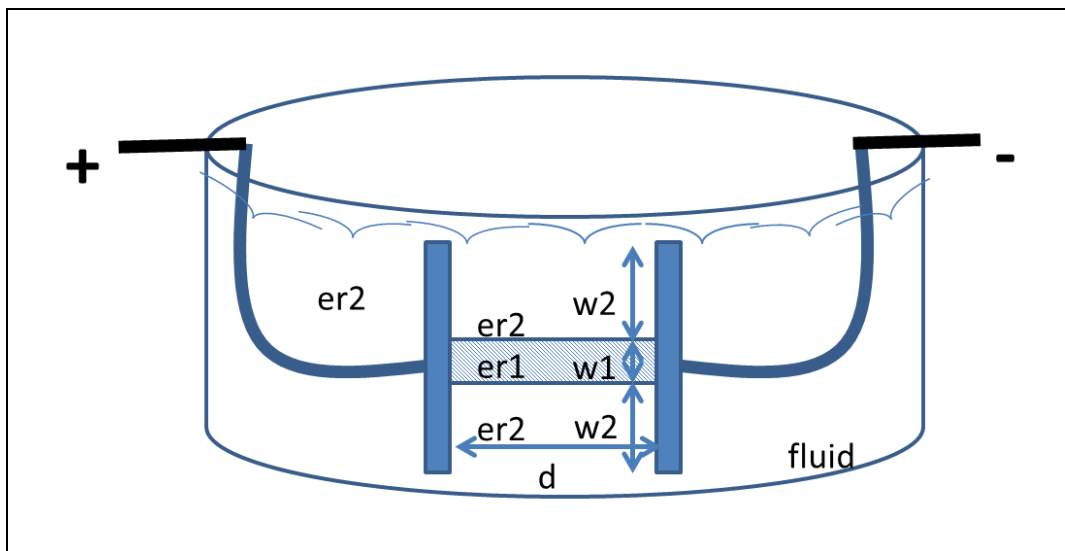


1. 50% - Determine the input impedance ( $Z_{in}$ ) of the above circuit. Next, design a matching circuit network (MN) using shunt stubs only match the input impedance ( $Z_{in}$ ) to a 50 ohm generator impedance at the position, new input impedance ( $Z_{in, NEW}$ ). All impedances are in ohms and the reference impedance is 50 ohms.



2. 50% - Determine the dielectric constant of an unknown solution ( $\epsilon_r2$ ) if the resonant frequency is 800 MHz using the capacitor model with the leads above is used. Assume the capacitor plate area is  $1 \text{ cm}^2$  and the plate separation ( $d$ ) is 1mm. The width ( $w1$ ) of the known dielectric ( $\epsilon_r1=4$ ) is 0.2 cm. The inductance associated with each lead is 1nH/lead, having a total system inductance of 2nH. In your solution, include a drawing of the equivalent circuit for this problem and define the individual and total capacitance values used to determine the unknown dielectric constant ( $\epsilon_r2$ ). The permittivity of air is  $8.85 \times 10^{-12} \text{ F/m}$ .

# The Complete Smith Chart

## Black Magic Design

