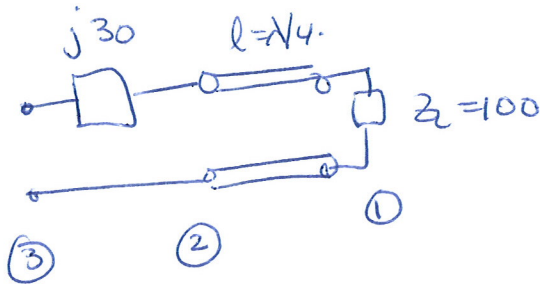


~~Problem 8~~ Question 1
Solutions #1

(1.0) a) $Z_{in} = ?$

① $Z_{in} = 100 \quad \bar{Z}_L = \frac{Z_L}{50} = 2$




② $\bar{Z}_2 = 0.5$

③ $j30 \Rightarrow j\frac{30}{50} = j0.6$

$\Rightarrow \bar{Z}_3 = 0.5 + j0.6$

$Z_3 = \bar{Z}_3 \times 50 = 25 + j30$

(1.0) b) Design the MN

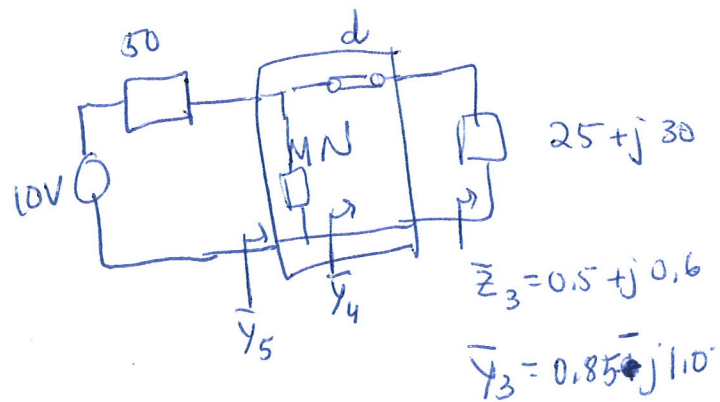

$d = (0.5 - 0.348)\lambda + 0.1645\lambda = (0.152 + 0.1642)\lambda = 0.3165\lambda$

$\bar{Y}_4 = 1 + j1.1$

Select \odot $+j1.1$ to offset $+j1.1$ in Y_4 .

Stub design:


Using an o.c. $l_{o.c.} = 0.368 \lambda$

Using a s.c. $l_{s.c.} = 0.118 \lambda$

~~Problem #1~~
Question

The Complete Smith Chart

Black Magic Design

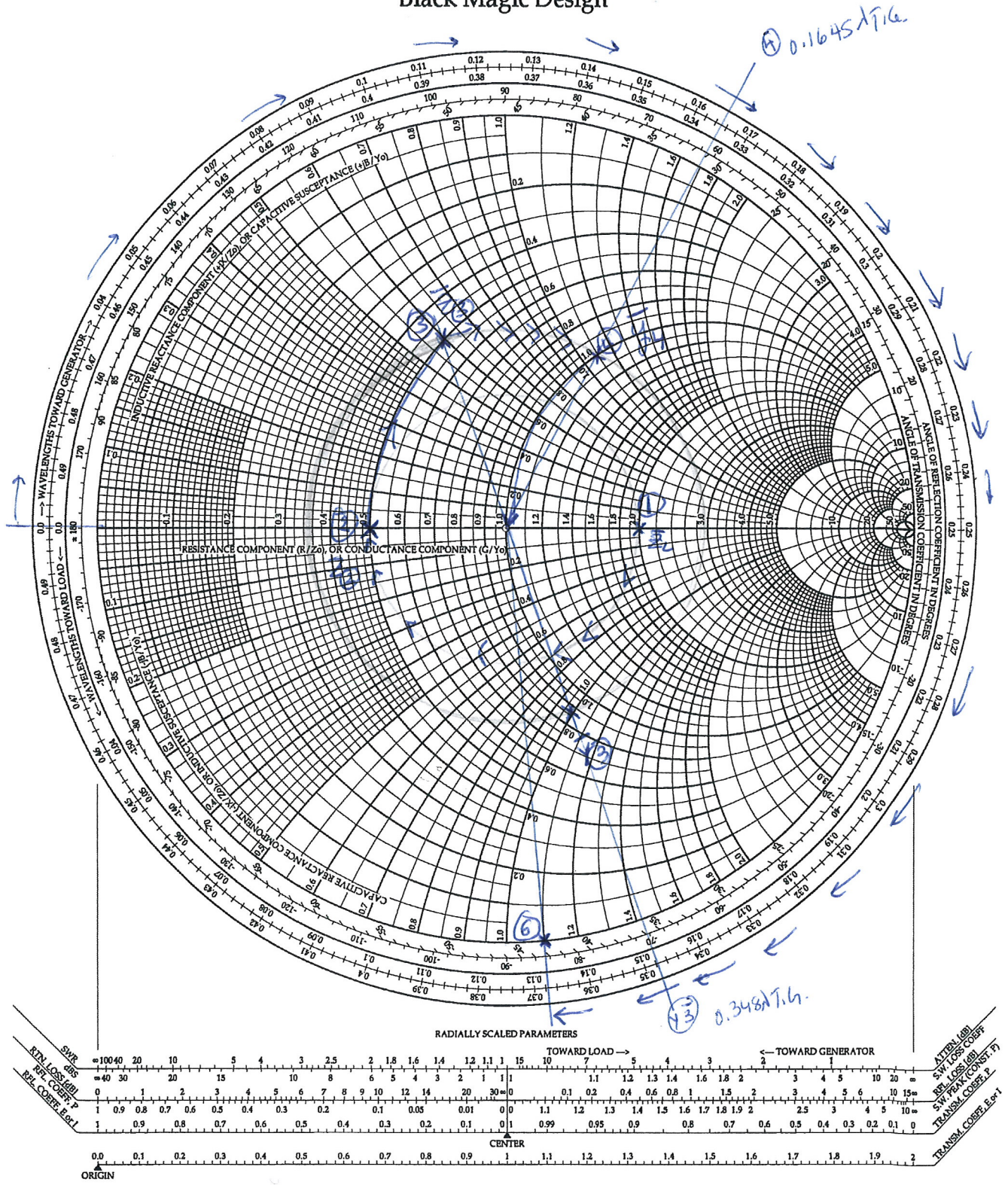

Question

Problem 8
Fields and Transmission Lines

Problem #2. - Solution #2

$$C_T = \frac{1}{L_T (2\pi f_r)^2}$$

$$f_r = 800 \text{ MHz}$$

$$L_T = 2 \times 10^{-9} \text{ H.}$$

$$C_T = \frac{1}{(2 \times 10^{-9})(2\pi \times 800 \times 10^6)^2}$$

$$= \frac{1}{5.05 \times 10^{10}}$$

$$(0.5) \quad C_T = 19.78 \text{ pF}$$

$$C_1 = \frac{\epsilon_{r1} \epsilon_0 A_1}{d} \quad A_1 = w_1 \times l_1$$

$$= (0.2 \times 10^{-2})(0.1 \times 10^{-2})$$

$$= \frac{4 \times 8.85 \times 10^{-12} \text{ F/m} \times (0.2 \times 10^{-2})(0.1 \times 10^{-2})}{1 \times 10^{-3}}$$

$$(0.5) \quad = 0.708 \text{ pF.}$$

$$(0.5) \quad C_2 = \frac{C_T - C_1}{1} = 9.54 \text{ pF} = \frac{\epsilon_{r2} \epsilon_0 A_2}{d}; \quad A_2 = 2w_2 \times l.$$

$$(0.5) \quad \epsilon_{r2} = \frac{C_2 d}{\epsilon_0 (2w_2)} = \frac{9.54 \times 10^{-12} \times (1 \times 10^{-3})}{8.85 \times 10^{-12} (2)(0.4 \times 10^{-2})(1 \times 10^{-2})} = 13.4.$$

$$\epsilon_{r2} = \frac{9.54 \times 10^{-12} + (-3) = -15}{0.4 \times 2 \times 8.85 \times 10^{-12} + (-2) + (-2)} = \frac{-15}{-16}$$

$$= \frac{1.34 \times 10^{-15}}{10^{-16}}$$

$$= 13.4 \times 10^1$$

$$\epsilon_{r2} = 13.4$$