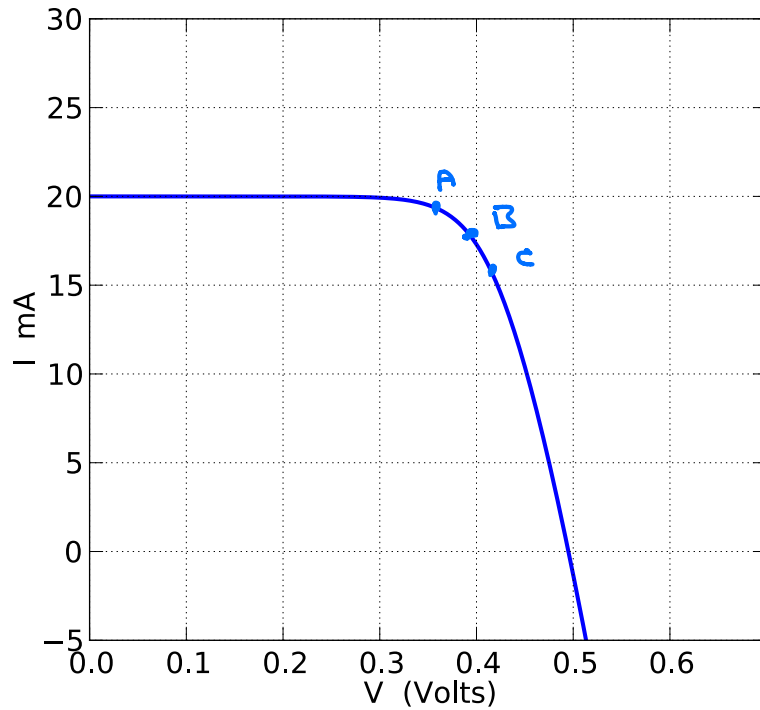


2. The IV characteristic of a photovoltaic cell is shown. Estimate the fill factor and the series resistance.



Need to find the maximum power point.

Method 1

Pick a few points and iterate. At the points shown

$$A: P = 0.35 \times 19 = 6.64 \text{ mW}$$

$$B: P = 0.39 \times 17.5 = 6.83 \text{ } \leftarrow \text{closest}$$

$$C: P = 0.42 \times 16 = 6.72$$


$$FF = \frac{P_{max}}{V_{oc} \cdot I_{sc}} = \frac{6.83}{(0.495) 20} = 0.69$$

Series R:

A rough estimate is

$$\frac{1}{R} = -\frac{dI}{dV} \Big|_{V_{oc}} = \frac{10}{0.05} \Rightarrow R = 5 \Omega$$

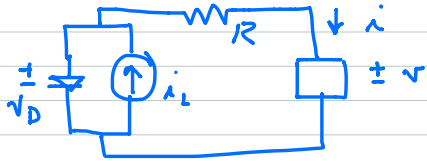This is too high. A better estimate is on next page.



$$v_D - v = iR$$

$$i = i_L - i_0 \left(e^{v_D/V_T} - 1 \right)$$

$$i = i_L - i_0 \left(e^{(v+iR)/V_T} - 1 \right)$$

$$\frac{di}{dv} = -i_0 \left(e^{\frac{v+iR}{V_T}} \right) \cdot \left(\frac{1}{V_T} + \frac{R}{V_T} \frac{di}{dv} \right)$$

$\approx -i_L$ near open circuit

$$\left. \frac{di}{dv} \right|_{V_{oc}} \left(1 + \frac{R i_L}{V_T} \right) = -\frac{i_L}{V_T}$$

$$\left. \frac{di}{dv} \right|_{V_{oc}} = \frac{-\frac{i_L}{V_T}}{1 + \frac{R i_L}{V_T}} = -\frac{1}{\frac{V_T}{i_L} + R}$$

$$\left(\left. \frac{di}{dv} \right|_{V_{oc}} \right)^{-1} = -\frac{V_T}{i_L} - R \Rightarrow R = -\frac{V_T}{i_L} - \left[\left. \frac{di}{dv} \right|_{V_{oc}} \right]^{-1}$$

In this case

$$R = -\frac{0.0259}{.020} + \left(\frac{0.010}{0.05} \right)^{-1} = \underline{\underline{3.71 \Omega}}$$

4. A p-n junction solar cell has $V_{oc} = 0.6$ V and $J_{sc} = 30$ mA/cm². A second cell, of the same area, has $V_{oc} = 0.7$ V and $J_{sc} = 12$ mA/cm². Assume that both cells obey the ideal diode equation,

a) Find the values of V_{oc} and J_{sc} when the two are connected in parallel?

b) Find the values of V_{oc} and J_{sc} when the two are connected in series?

a) In parallel, $J_{sc} = 12 + 30 = 42$ mA/cm².

$$J_{01} = \frac{J_{sc1}}{(e^{V_{oc1}/V_T} - 1)} = 2.61 \times 10^{-9} \text{ and } J_{02} = 2.2 \times 10^{-11}$$

$$\text{so } J = J_{sc} + (J_{01} + J_{02})(e^{V/V_T} - 1) = 42 + 2.63 \times 10^{-9} (e^{V/V_T} - 1)$$

$$\Rightarrow V_{oc} = V_T \ln\left(\frac{42}{2.63 \times 10^{-9} + 1}\right) = 0.61 \text{ V}$$

b) Series

$$V_{oc} = 0.6 + 0.7 = 1.3 \text{ V}$$

$$J_{sc} = 12 \text{ mA/cm}^2 \text{ (series limit)}$$