

Fall 2015
 Problem 9
 Power Systems & Power Electronics Solution

Problem 9(a)

In a Flyback converter operating in steady state, $V_m = 48V$, duty-ratio $D = 0.385$, $N_1/N_2 = 6$, the magnetizing inductance $L_m = 150\mu H$, and the switching-frequency $f_s = 200kHz$. Neglect the leakage inductances and assume this converter to be lossless. Assume the output voltage to be ripple-free.

(a) This converter is operating at the output power P_o at which the flux in the core is at the border of incomplete-demagnetization and the complete-demagnetization modes (similar to the border of continuous and the discontinuous current-conduction modes in non-isolated dc-dc converters).




1. Calculate the output voltage V_o .
2. Calculate and draw the waveforms of the input current, and the current supplied to the output stage consisting of the parallel combination of the output capacitor and the load-resistance.
3. Calculate the output power P_o .

(b) If this converter is operating at double the power calculated in part (a), calculate the following:

1. The output voltage V_o .
2. Calculate and draw the waveforms of the input current, and the current supplied to the output stage consisting of the parallel combination of the output capacitor and the load-resistance.

Solution

(a)

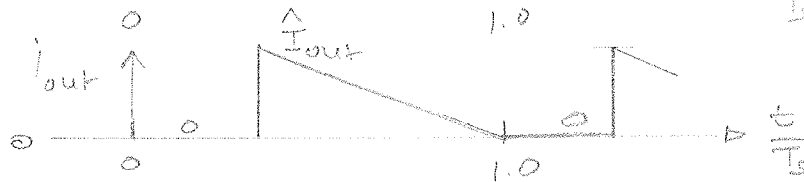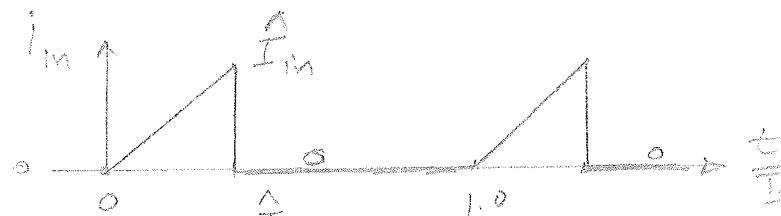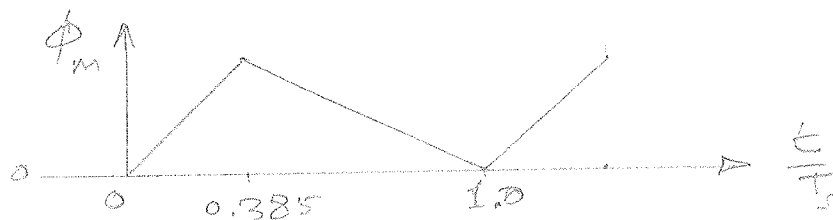

$$V_o = \frac{N_2}{N_1} \frac{D}{1-D} V_{in} = 5V$$

$$I_{in}(0) = 0 \quad \hat{I}_{in} = \frac{48 \times 0.385 \times 5\mu}{150\mu} = 0.616A$$

$$I_{in(avg)} = \frac{1}{2} \hat{I}_{in}(0.385) = 0.1186A$$

$$P_o = 48 \times 0.1186 = 5.69W$$

$$\hat{I}_{out} = 6 \times 0.616A = 3.696A$$

(b)

$$P_o = 2 \times 5.69 = 11.38 \text{ W}$$

$$V_o = 5 \text{ V}$$


$$I_{in}(\text{avg}) = \frac{11.38}{48} = 0.237 \text{ A}$$

$$\hat{I}_{in} - I_{in}(0) = \frac{48 \times 0.385 \times 5 \mu}{150 \mu} = 0.616 \text{ A}$$

$$\therefore I_{in}(0) = 0.3076 \text{ A}, \quad \frac{\hat{I}_{in}}{I_{in}(0)} = 0.9235$$

$$\hat{I}_{out} = 6 \hat{I}_{in} = 5.5416 \text{ A}$$
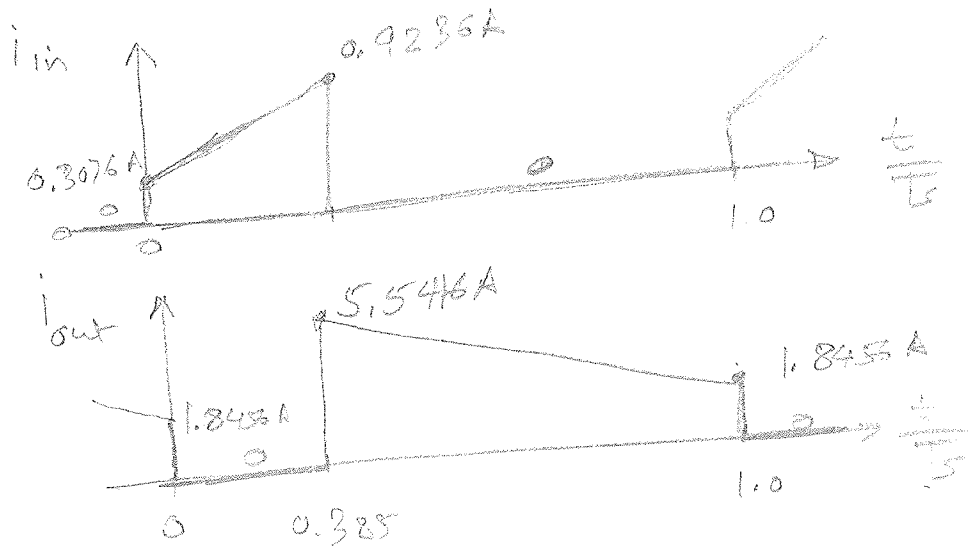
$$I_{out}(0) = 6 \times I_{in}(0) = 1.8456 \text{ A}$$



Problem 9 (b) Suppose an industrial plant is served from a three-phase 208 V (RMS line-line) transformer. The real power demand of the plant is 80 kW at a power factor of 0.5 (lag).

- (i) Find the apparent power and RMS line current magnitude.

$$\begin{aligned}P_{3\phi} &= 80 \text{ kW} \\ &= \sqrt{3}V_{LL}I_L \cos \theta \\ &= S_{3\phi} \cos \theta \\ \Rightarrow S_{3\phi} &= \frac{80 \text{ kW}}{0.5} = 160 \text{ kVA} \\ I_L &= \frac{80}{\sqrt{3}(208)(0.5)} = 444 \text{ A}\end{aligned}$$

- (ii) Suppose the power factor is corrected to 0.9 (lag) with capacitor banks. Find the new apparent power and RMS line current magnitude.

$$\begin{aligned}S_{3\phi} &= \frac{80 \text{ kW}}{0.9} \\ &= 88.9 \text{ kVA} \\ I_L &= \frac{80}{\sqrt{3}(208)(0.9)} = 247 \text{ A}\end{aligned}$$

- (iii) Suppose the line losses before power factor correction were 4 kW. What are the line losses after power factor correction?

$$\begin{aligned}\frac{P_{loss,before}}{P_{loss,after}} &= \frac{I_{L,before}^2}{I_{L,after}^2} \\ \Rightarrow P_{loss,after} &= 4 \text{ kW} \times \frac{247^2}{444^2} \\ &= 1.24 \text{ kW}\end{aligned}$$