

Problem 9 (a) In a Flyback converter operating in steady state, the input voltage, $V_{in} = 48$ V, duty-ratio, $D = 0.385$, turns ratio, $N_1/N_2 = 6$, the magnetizing inductance, $L_{m1} = 150$ μ H, and the switching frequency, $f = 200$ kHz. Neglect the leakage inductances and assume this converter to be lossless. Assume the output voltage to be ripple-free.

- (i) This converter is operating at the output power at which the flux in the core is at the border of incomplete-demagnetization and the complete-demagnetization modes (similar to the border of continuous and the discontinuous current-conduction modes in non-isolated dc-dc converters).
 - (a) Compute the output voltage, V_o .
 - (b) Calculate and draw the waveforms of the input current, and the current supplied to the output stage consisting of the parallel combination of the output capacitor and the load-resistance.
 - (c) Calculate the output power, P_o .
- (ii) If this converter is operating at one-half the power calculated in part (i), calculate the following:
 - (a) Calculate the output voltage, V_o .
 - (b) Calculate and draw the waveforms of the input current, and the current supplied to the output stage consisting of the parallel combination of the output capacitor and the load-resistance.

(2 P o i n t s)

Problem 9 (b) Suppose an industrial plant is served from a three-phase 208 V (RMS line-line) transformer. The real power demand of the plant is 80 kW at a power factor of 0.5 (lag).

- (i) Find the apparent power and RMS line current magnitude.
- (ii) Suppose the power factor is corrected to 0.9 (lag) with capacitor banks. Find the new apparent power and RMS line current magnitude.
- (iii) Suppose the line losses before power factor correction were 4 kW. What are the line losses after power factor correction?