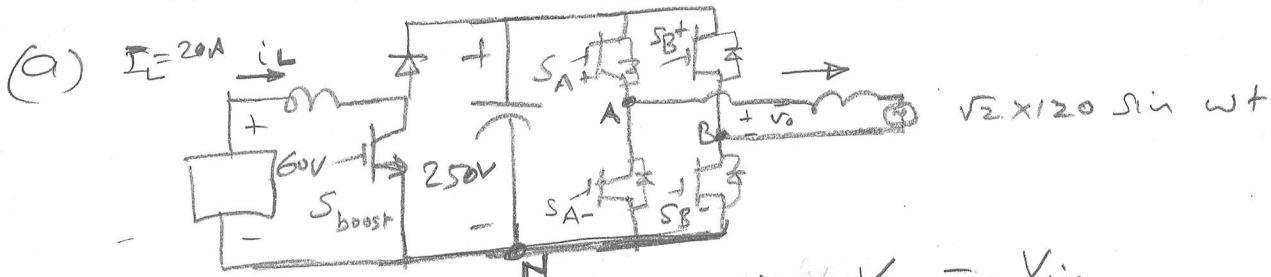


Problem 9b (2 points)

A Photovoltaic panel under a given insolation condition operates at its maximum power point with the voltage of 60 V and the current of 20 A. This PV panel supplies power to a 120-V, 60-Hz, residential grid. The PV interface consists of a boost dc-dc converter, followed by a full-bridge, single-phase, dc-ac inverter. Assume all components to be ideal (i.e., zero power loss everywhere for the sake of simplicity).

The output of the boost dc-dc converter, operating in a continuous-current-conduction mode at a switching frequency of 250 kHz, is 250 V (dc) across a very large dc-link capacitor such that the ripple in the capacitor voltage can be assumed to be negligible. This capacitor voltage acts as the input to a single-phase, full-bridge, inverter that supplies power to the grid at a unity power factor; assume the ripple in the output current to be negligible. Inverter switches are sine-PWM controlled with the switching frequency of 100 kHz. Assume the inductance on the ac-side of the inverter to be negligible.

- Draw the circuit diagram of such an interface and label all the components.
- What is the duty-ratio of the transistor-switch in the boost dc-dc converter?
- In the single-phase inverter, over one switching time-period, plot the duty-ratios, each below the other, of all the four transistor-switches as functions of time when the grid voltage is at its positive peak. Label your plots with appropriate numerical values.
- What is the peak value of the current into the residential grid?



(b)

$$\frac{V_o}{V_{in}} = \frac{1}{1 - D_{boost}} \quad \therefore V_o - D_{boost} V_o = V_{in}$$

$$D_{boost} = \frac{V_o - V_{in}}{V_o} = 1 - \frac{V_{in}}{V_o} = 1 - \frac{60}{250} = 0.76$$

(c)

$$\bar{V}_o = \sqrt{2} \times 120 \sin \omega t = 169.7 \sin \omega t$$

$$\bar{V}_{AN} = \frac{V_{dc}}{2} + \frac{\bar{V}_o}{2}, \quad \bar{V}_{BN} = \frac{V_{dc}}{2} - \frac{\bar{V}_o}{2}$$

$$d_{SA+} = \frac{\bar{V}_{AN}}{V_{dc}} = \frac{1}{2} + \frac{1}{2} \frac{\bar{V}_o}{V_{dc}} = \frac{1}{2} + \frac{1}{2} \frac{169.7}{250} = 0.839$$

$$d_{SA-} = 1 - d_{SA+} = 1 - 0.84 = 0.161$$

$$d_{SB+} = \frac{\bar{V}_{BN}}{V_{dc}} = \frac{1}{2} - \frac{1}{2} \frac{\bar{V}_o}{V_{dc}} = 0.161$$

$$d_{SB-} = 1 - d_{SB+} = 0.839$$

(d)

$$P = 60 \times 20 = 1,200 \text{ W}$$

$$I_{Peak} = \sqrt{2} \frac{1200}{120} = 14.14 \text{ A}$$

PhD Preliminary Written Exam  
Spring 2015

Problem 9  
Power Systems

Page 2 of 2  
Solution

**Problem 9 (b)** A synchronous machine is connected to an infinite bus as shown in the figure below. The machine has the following parameters: synchronous speed,  $\omega_s = 120\pi$  [rad/s], inertia constant,  $H = 8$  [s], machine damping,  $D = 0.004$  [rad<sup>-1</sup>s], machine terminal voltage,  $E = 0.9$  [pu], mechanical power input,  $P_M = 1.0$  [pu], machine terminal impedance,  $X_M = 0.2$  [pu], the infinite bus voltage magnitude,  $v_\infty = 1.0$  [pu], and the line impedance,  $X_L = 0.25$  [pu]. Recall that the *swing equations* that govern the evolution of the rotor angle,  $\delta$ , and frequency,  $\omega$ , are given by:

$$\begin{aligned} \frac{d\delta}{dt} &= \omega - \omega_s, \\ \frac{2H}{\omega_s} \frac{d\omega}{dt} &= P_M - P_E - D(\omega - \omega_s), \end{aligned} \quad (1)$$

where  $P_E$  is the electrical output power sourced by the generator from terminal 1.

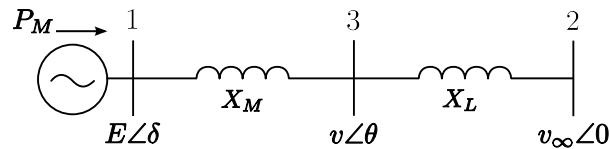


Figure 1: Single line diagram of single machine infinite bus

**Solution 9 (b)**

- (i) Write an expression for the electrical output power,  $P_E$ . Your expression should only be a function of  $E$ ,  $v_\infty$ ,  $\delta$ ,  $X_M$ , and  $X_L$ .

**Solution:**

$$P_E = \frac{E v_\infty}{X_M + X_L} \sin \delta \quad (2)$$

- (ii) Find the equilibrium points for the system in (1) in the interval,  $[0, \pi]$ .

**Solution:**

Swing equations are given by:

$$\begin{aligned} \frac{2H}{\omega_s} \frac{d^2\delta}{dt^2} + D \frac{d\delta}{dt} &= P_M - P_E, \\ \rightarrow 0.0424 \frac{d^2\delta}{dt^2} + 0.004 \frac{d\delta}{dt} &= 1 - 2 \sin \delta \end{aligned}$$

$$\begin{aligned} 1 - 2 \sin \bar{\delta} &= 0 \\ \rightarrow \bar{\delta} &= \frac{\pi}{6}, \frac{5\pi}{6} \end{aligned}$$

- (iii) Linearizing the system around the equilibrium point, find the eigenvalues.

**Solution:**

$$x_1 = \delta, \quad x_2 = \frac{d\delta}{dt}$$

Then,

$$\begin{bmatrix} \dot{x}_1 \\ \dot{x}_2 \end{bmatrix} = \begin{bmatrix} x_2 \\ \frac{1}{0.0424} (1 - 2 \sin x_1 - 0.004x_2) \end{bmatrix}$$

Linearization around the equilibrium point,  $\bar{x}_1$ , is:

$$\begin{bmatrix} \dot{x}_1 \\ \dot{x}_2 \end{bmatrix} \simeq \begin{bmatrix} 0 & 1 \\ -\frac{2}{0.0424} \cos x_1 & -0.004 \end{bmatrix} \begin{bmatrix} x_1 \\ x_2 \end{bmatrix}$$

Linearization around the equilibrium points,  $\bar{x}_1 := \bar{\delta} = \frac{\pi}{6}$ , yields:

$$\begin{bmatrix} \dot{x}_1 \\ \dot{x}_2 \end{bmatrix} \simeq \begin{bmatrix} 0 & 1 \\ -40.8503 & -0.0943 \end{bmatrix} \begin{bmatrix} \Delta x_1 \\ \Delta x_2 \end{bmatrix}$$

Linearization around the equilibrium points,  $\bar{x}_1 := \bar{\delta} = \frac{5\pi}{6}$ , yields:

$$\begin{bmatrix} \dot{x}_1 \\ \dot{x}_2 \end{bmatrix} \simeq \begin{bmatrix} 0 & 1 \\ 40.8503 & -0.0943 \end{bmatrix} \begin{bmatrix} \Delta x_1 \\ \Delta x_2 \end{bmatrix}$$

(iv) Mention which equilibrium point is stable.

**Solution:**

Eigenvalues for the equilibrium point,  $\bar{x}_1 := \bar{\delta} = \frac{\pi}{6}$ , are  $\lambda_{1,2} = -0.0471 \pm j6.3913$ , which is stable. Eigenvalues for the equilibrium point,  $\bar{x}_1 := \bar{\delta} = \frac{5\pi}{6}$ , are  $\lambda_{1,2} = 6.3444, -6.4387$ , which is unstable.