

## Problem 4 - Analog and Digital Electronics - Solutions

a) For  $I_{D3}$ :

$$I_{D3} = \frac{1}{2} k_n' \left(\frac{W}{L}\right)_3 (V_{GS3} - V_T)^2 = 3 \times 10^{-4} (V_{GS3} - 1)^2$$

$$I_{D3} \cdot 30k + V_{GS3} = 20$$

$$\text{Solving for } V_{GS3}: 9V_{GS3}^2 - 17V_{GS3} - 11 = 0$$

$$\Rightarrow V_{GS3} = 2.4 \text{ V.}$$

$$\therefore I_{D3} = I_{D4} = 0.587 \text{ mA}$$

$$I_{D1} = I_{D2} = \frac{I_{D4}}{2} = 0.293 \text{ mA.}$$

$$\therefore V_o = 10 - I_{D2} 16k = 5.31 \text{ V.}$$

b)  $A_o = \frac{1}{2} g_{m1} R_{D1}$

$$g_{m1} = \sqrt{2k_n' \left(\frac{W}{L}\right)_1 I_{D1}} = 0.34 \text{ mA/V}$$

$$\therefore A_o = 2.72$$

c)  $A_{cm} = - \frac{R_{D1} g_{m1}}{1 + 2g_{m1} R_{O4}} \approx - \frac{R_{D1}}{2R_{O4}}$

$$R_{O4} = \frac{1}{\lambda_4 I_{D4}} = 170 \text{ k}\Omega$$

$$\therefore A_{cm} \approx -0.0467$$

## Problem 4 - Analog and Digital Electronics - Solutions

$$d) \text{ CMRR} = 20 \log \frac{|A_{od}|}{|A_{cml}|} = 35.3 \text{ dB}$$

e)  $V_{in\max}$  occurs when  $Q_1 + Q_2$  are at the edge of saturation,

$$\text{i.e., } V_{GS1} = V_t, \quad V_{DS1} = V_{OV1}$$

$$\therefore V_{GS1} = 1 = V_{in\max} - V_G = V_{in\max} - (10 - I_{D1}(k))$$

$$\therefore V_{in\max} = 6.31 \text{ V}$$

$V_{in\min}$  occurs when  $Q_4$  is at edge of saturation,

$$\text{i.e., } V_{GS4} = V_t, \quad V_{DS4} = V_{OV4}$$

$$\text{Now } V_{OV4} = V_{GS4} - V_t = 2.4 - 1 = 1.4$$

$$\therefore V_{in\min} = V_{GS1} + V_{DS4} - 10$$

$$\text{But } V_{GS1} = \sqrt{\frac{I_{D1}}{\frac{1}{2}k_n' \left(\frac{W}{L}\right)_1}} + V_t = 2.71 \text{ V}$$

$$\therefore V_{in\min} = -5.89 \text{ V}$$

$$\therefore -5.89 \text{ V} \leq V_{in} \leq 6.31 \text{ V}$$