

In the amplifier circuit below, the transistors are in saturation and have the following characteristics:

$$K_n' = \mu_n C_{ox} = 2 \times 10^{-5} \text{ A/V}^2$$


$$(W/L)_1 = (W/L)_2 = 10$$

$$(W/L)_3 = (W/L)_4 = 30$$

$$V_t = 1 \text{ V}$$

$$\lambda_1 = \lambda_2 = \lambda_3 = 0$$

$$\lambda_4 = 0.01 \text{ V}^{-1}$$

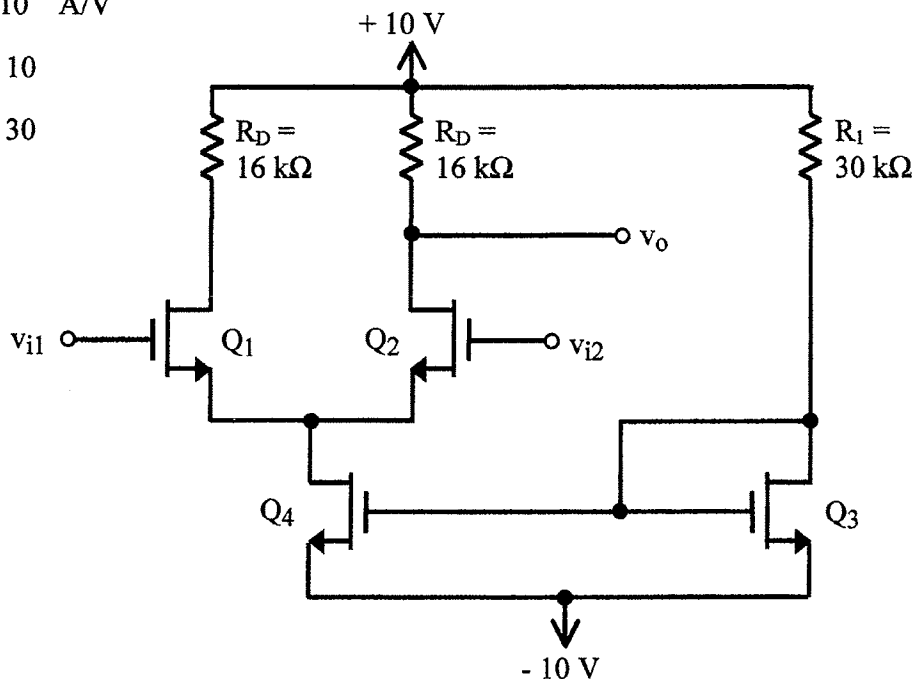

- For this amplifier, determine the dc bias point value for  $v_o$ . (0.5 points)
- What is the small signal single-ended voltage gain  $A_o = v_o / (v_{i1} - v_{i2})$  for this amplifier? (1 point)
- What is the small signal common mode voltage gain  $A_{cm} = (v_o / v_{icm})$  for this amplifier, where  $v_{i1} = v_{i2} = v_{icm}$ ? (1 point)
- What is the CMRR for this single-ended amplifier? (0.5 points)
- If the output is connected directly to the inverting input and the input voltage is applied to the non-inverting input, forming a voltage follower, determine the range of input voltages over which the circuit will function correctly as a voltage follower. Note that this range of allowable input voltages is often called the input common-mode range. (1 point)