

Prob 9 a Power Systems Solution

a) Tie Flow

$$\text{Area 1} \quad \text{Total Gen} = P_1 + P_2 = 200 + 300 = 500 \text{ mw}$$

$$\text{Area 1} \quad \text{Load} = L_1 + L_2 = 550 + 50 = 600$$


$$\text{Area 2} \quad \text{Gen} = P_3 + P_4 = 300 + 300 = 600$$

$$\text{Area 2} \quad \text{Load} = L_3 + L_4 = 50 + 450 = 500$$

Area 1 has Net deficit of 100 mw (gen < load)

Area 2 " " " Surplus " " " (gen > load)

Tie Flow is 100 mw area 2 to area 1

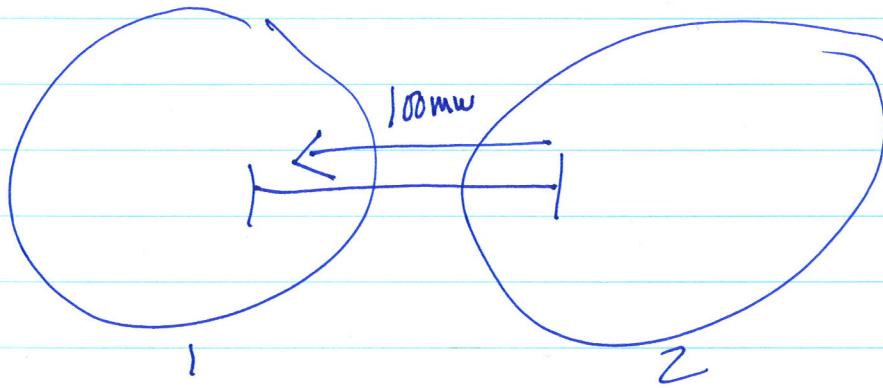

Prob 9a Solution

b) Tie line opened.

Area 1 has more load than gen
so its freq. will drop
Load 2 will be dropped off.

Area 2 has more gen than load
so its frequency will rise
load 3 will remain connected

Result:

$$\text{Area 1 } P_1 + P_2 = 500 \text{ MW}$$

$$\text{load} = L_1 = 550 \text{ MW}$$

Frequency will still be dropping.

$$\text{Area 2 } P_3 + P_4 = 600 \text{ MW}$$

$$\text{load} = L_3 + L_4 = 580 \text{ MW}$$

Frequency is rising,

Area 1

$$\Delta P_{\text{gen}} = +50 \text{ MW} = \Delta P_1 + \Delta P_2$$

Switch $\Delta \beta^1$ to pu.



$$+50 = \left(-\frac{1}{R_1} + \frac{1}{R_2} \right) \Delta f_1$$

$$\Delta f_1 = \frac{+.5}{-\left(\frac{1}{R_1} + \frac{1}{R_2}\right)} \quad (\Delta P \text{ in pu})$$

$$= \frac{.5}{-(10.66)} = -.0468 \%$$

Prob 9a Solution
b) cont

Area 2

$$\Delta P_{\text{gen}} = \Delta P_3 + \Delta P_4 = -100 \text{ MW} = -1.0 \text{ pu}$$

$$-1.0 = \left(\frac{-1}{Y_{R3}} + \frac{-1}{Y_{R4}} \right) \Delta f_2$$

$$\Delta f_2 = \frac{1.0}{(Y_{R3} + Y_{R4})} = \frac{1}{70} = .0142 \text{ %}$$

Final Generation:

$$\Delta P_1 = \frac{-1}{R_1} (\Delta f_1) = \frac{-1}{.15} (-.0468 \%) = .3125 \text{ pu}$$

$$\Delta P_2 = \frac{-1}{R_2} (\Delta f_1) = \frac{-1}{.25} (-.0468 \%) = .1872 \text{ pu}$$

Net increase .5 pu

$$\Delta P_3 = \frac{-1}{R_3} (\Delta f_2) = \frac{-1}{.05} (.0142 \%) = -.284 \text{ pu}$$

$$\Delta P_4 = \frac{-1}{R_4} (\Delta f_2) = \frac{-1}{.02} (.0142 \%) = -.71 \text{ pu}$$


Net decrease 1.0 pu

New Gen Values in MW

$$P_1 = 200 + 31.25 = 231.5 \text{ MW} \quad P_2 = 300 + 18.7 = 318.7 \text{ MW}$$

$$P_3 = 300 - 28.4 = 271.6 \quad P_4 = 300 - 71. = 229 \text{ MW}$$

Prob 9 b solution

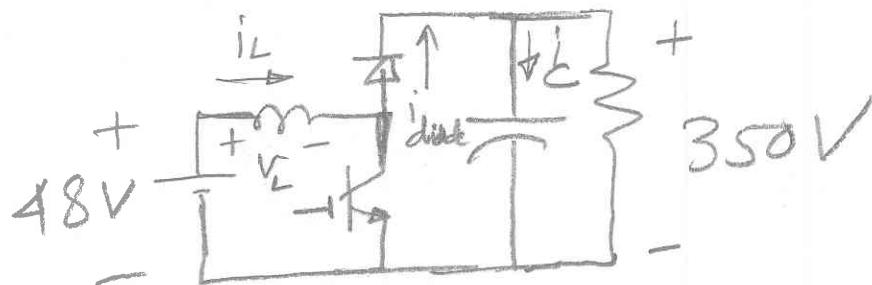

$$f_s = 200 \text{ kHz}, T_s = 5 \mu\text{s}$$

$$P_{max} = 120 \text{ W} \quad P_{max}/3 = 40 \text{ W}$$

$$@ P_{max}: \quad I_{in} = \frac{120}{48} = 2.5 \text{ A}$$

$$I_o = \frac{120}{350} = 0.3529 \text{ A}$$

$$(a) @ P_0 = \frac{P_{max}}{3} = 40 \text{ W}$$

$$I_{L_{avg}} = I_{in} = \frac{40}{48 \text{ V}} = 0.833 \text{ A}$$

$$I_{p-p} = 2 \times I_{L_{avg}} = 2 \times 0.833 = 1.666 \text{ A}$$

$$\frac{V_o}{V_{in}} = \frac{1}{1-D} = \frac{350}{48} \Rightarrow D = 0.8629$$


$$L \frac{\Delta I}{\Delta T} = V \quad \therefore L = \frac{V_{in} D T_s}{I_{p-p}}$$

$$= \frac{48 \times 0.8629 \times 5}{1.666} \text{ mH}$$

$$= 124.31 \text{ mH}$$

$$I_o = \frac{40 \text{ W}}{350 \text{ V}} = 0.1143 \text{ A}$$

(b)

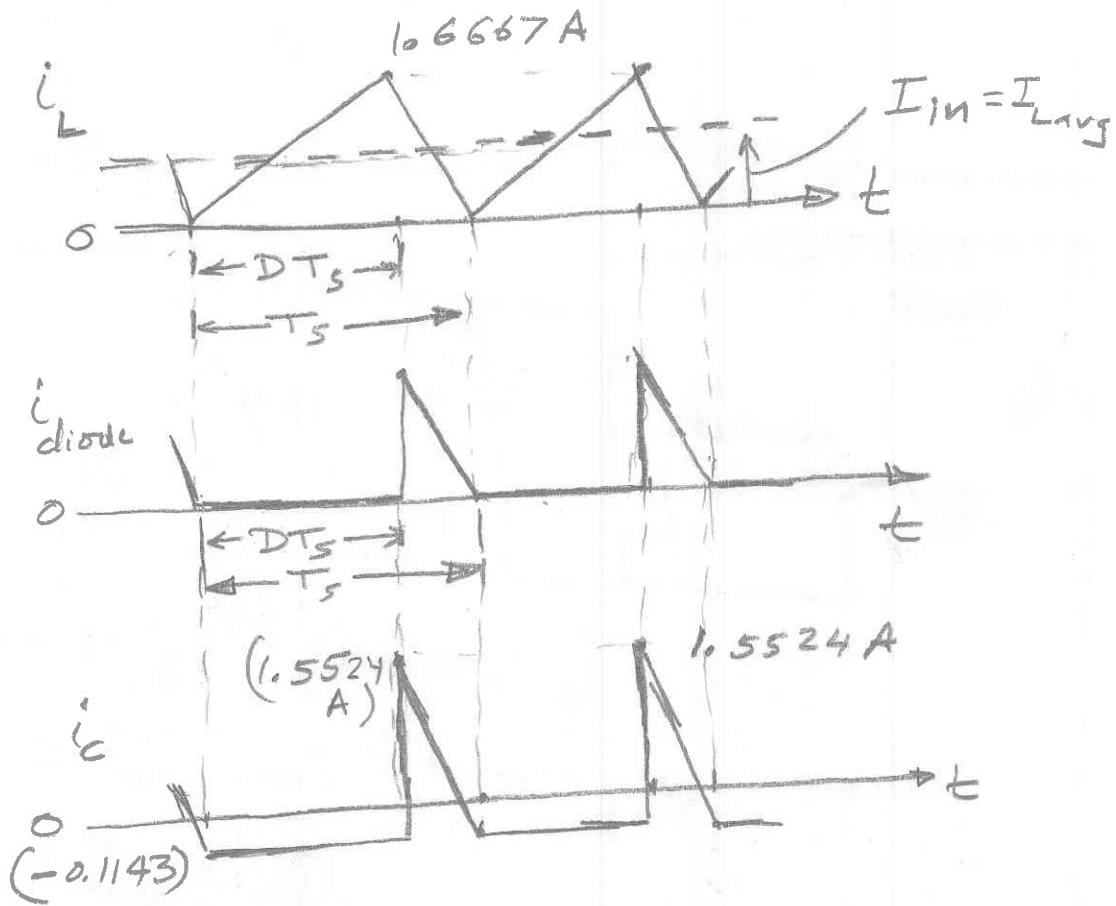

$$\begin{aligned}
 I_{C, \text{peak}} &= I_{\text{diode, peak}} - I_o \\
 &= 1.6667 - 0.1143 \\
 &= 1.5524 \text{ A}
 \end{aligned}$$