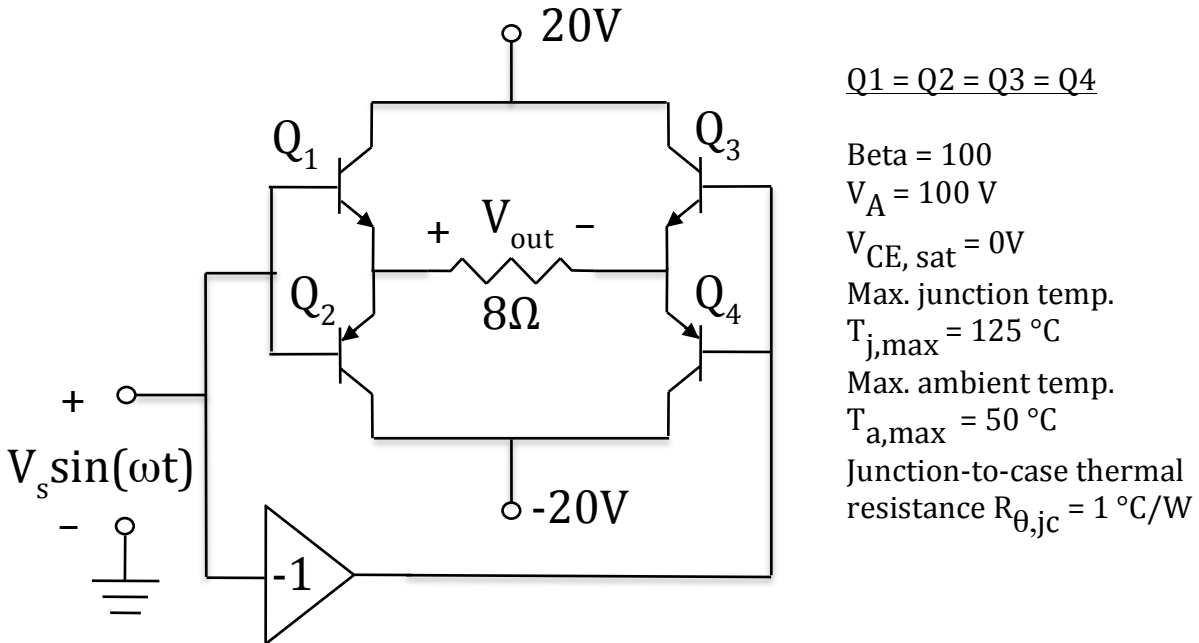


The amplifier shown below is termed a bridge amplifier. The amplifier symbol with the -1 inside is an inverting amplifier with unity gain. The BJT characteristics are shown next to the circuit diagram.



- (0.5 points)  
Estimate the maximum average power the circuit can deliver to the 8 ohm load.
- (1 point)  
What is the efficiency ( $\langle P_{\text{load}} \rangle / \langle P_{\text{supplies}} \rangle$ ) at maximum output signal swing?
- (0.5 points)  
What should be the peak voltage rating and current rating of the transistors. Include a 50% factor of safety.
- (1 point)  
What is the maximum average power dissipated in a transistor?
- (1 point)  
The transistors are mounted next to each other on a common heat sink. Specify the required heat sink thermal resistance so that  $T_{j, \text{max}}$  is not exceeded when the ambient is at  $50^\circ\text{C}$ .


# PhD Prelim, Exam Solutions

Analog/Digital Electronics

Sp 2014

$$\textcircled{1} \quad \langle P_{\text{Load}} \rangle = \frac{V_o^2}{2R_L} \quad V_{o|\text{max}} = 40 \text{ V b-p}$$
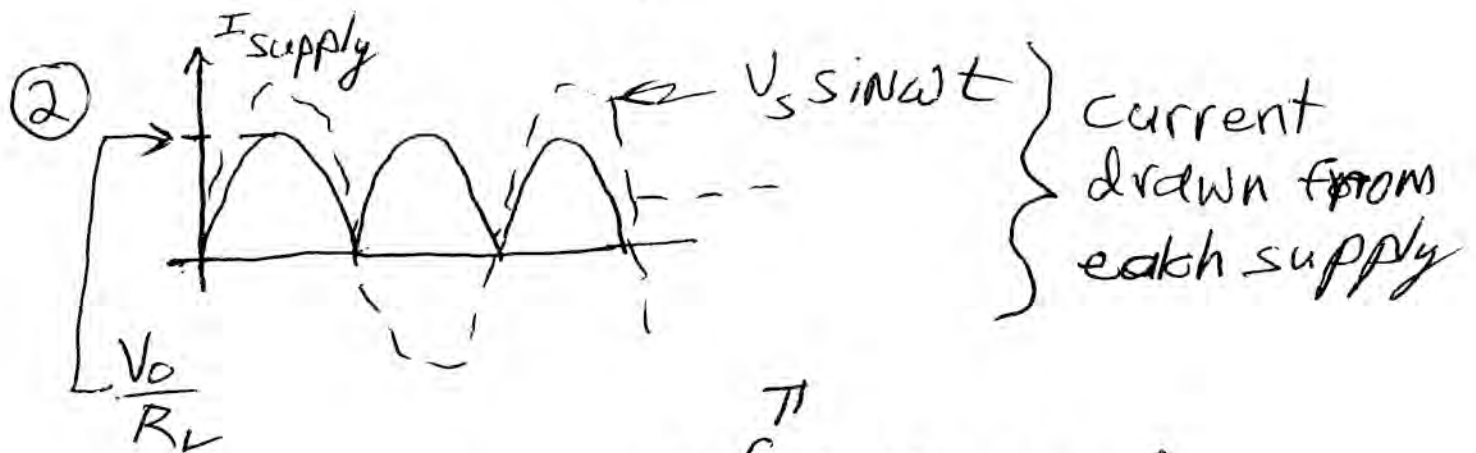
$$\langle P_{\text{load}} \rangle_{\text{max}} = \frac{(40)^2}{(2)(8)} = \frac{1600}{16} = \boxed{100 \text{ watts}}$$



$$\langle P_{\text{supplies}} \rangle = 2 \frac{1}{\pi} \int_0^{\pi} V_{CC} \frac{V_o}{R_L} \sin \theta d\theta$$

$$= \frac{2}{\pi} V_{CC} \frac{V_o}{R_L} \left[ -\cos \theta \right]_0^{\pi}$$

$$= \frac{2}{\pi R_L} V_{CC} V_o \left[ -(-1) - (-1) \right]$$

$$\langle P_{\text{supplies}} \rangle = \frac{4V_{CC} V_o}{\pi R_L}$$

At max signal swing  $V_o = 2V_{CC}$  base-to-peak

$$\text{Efficiency}_{\max} = \frac{(2V_{CC})^2}{2R_L \frac{(4V_{CC})(2V_{CC})}{\pi R_L}}$$
$$= \frac{4\pi}{16} = \boxed{\frac{\pi}{4} \sim 79\%}$$

③ Max.  $V_{CE}$  imposed by circuit = 40V

$$\text{Voltage rating} = 40 \times 1.5 = \boxed{60V}$$

Max collector current  $\xrightarrow{\text{factor of safety}}$

$$= \frac{40V}{8\Omega} = 5A$$

$$\text{current rating} = (5)(1.5) = \boxed{7.5A}$$

④  $\langle P_{\text{trans}} \rangle = \frac{\langle P_{\text{supplies}} \rangle - \langle P_{\text{load}} \rangle}{4}$

= pwr dissipated in each transistor

$$\langle P_{\text{trans.}} \rangle = \frac{4V_{CC}V_0}{4R_L\pi} - \frac{V_0^2}{(4)(2R_L)}$$

$$\frac{d\langle P_{\text{trans.}} \rangle}{dV_0} = 0 = \frac{V_{CC}}{\pi R_L} - \frac{V_0}{4R_L}$$

$$V_0 = \frac{4}{\pi} V_{CC} = \text{value of } V_0 \text{ at max. pwr dissipation in BJTs}$$

$$\langle P_{\text{trans.}} \rangle \Big|_{\text{max}} = \frac{4V_{CC}}{4\pi R_L} \times \frac{4V_{CC}}{\pi} - \left( \frac{4V_{CC}}{\pi} \right)^2 \frac{1}{8R_L}$$

$$= \frac{16V_{CC}^2}{4\pi^2 R_L} \left[ 1 - \frac{1}{2} \right]$$

$$= \frac{2}{\pi^2} \frac{V_{CC}^2}{R_L} = \frac{2}{10} \frac{100}{8}$$

$$\langle P_{\text{trans.}} \rangle \Big|_{\text{max}} = 10 \text{ watts}$$

$$\textcircled{5} T_{j,\text{max}} = 4 \langle P_{\text{trans.}} \rangle \Big|_{\text{max}} \left[ R_{\theta,jc} + R_{\theta,sa} \right] + T_{a,\text{max}}$$

$$R_{\theta,sa} = \frac{[25-50]}{(4)(10)} - 1 = 0,88 \text{ } ^\circ\text{C/W}$$