

Solutions

(a) Note that a 3-to-8 decoder and a single AND gate can implement any Boolean function of 3 variables. So the strategy is to find an analytic expression for the given function (of 5 variables) and try to simplify it, so that it can be implemented using a decoder, using additional flexibility provided by Enable input (of the decoder).

Hence, solution to this problem requires two parts:

- (1) Deriving an analytic expression for the Boolean function $F(A,B,C,D,E)$ shown on K-map, in a min SOP or min POS form.
- (2) Implementing this Boolean function using the decoder.

Part (1). The decoder specified in this problem has 3 inputs and inverted outputs; therefore it can implement any Boolean function of 3 variables in a maxterm canonical form, where selected decoder outputs (maxterms) are used as inputs to a single AND gate. Hence, a reasonable solution strategy is to find a simple expression for the Boolean function in a minimum Product-of-Sums (POS) form.

The 5-variable function shown on K-map is (almost) symmetric with respect to C, i.e. all maxterms in the right half (for $C=1$) are also present in the left half of the map (for $C=0$). In addition, the left half has an extra maxterm $(A+B+C+D+E')$.

So we can first simplify the symmetric part in a min POS form, and then add an extra product term (the extra maxterm), to form the function $F(A,B,C,D,E)$.

Note that the symmetric part of the K-map is a function of 3 variables, because its maxterms are symmetric with respect to both C and A variables. So its min POS form is a 3-variable function $G(B,D,E) = (B+D'+E')(B'+E)$ – can be found from K-map.

The original 5-variable function can be decomposed as

$$F(A,B,C,D,E) = (A+B+C+D+E') G(B,D,E) \text{ or, even better/simpler as } \\ F(A,B,C,D,E) = (A+B+C+E') G(B,D,E)$$

Part (2). Function $G(B,D,E)$ can be implemented using a decoder with inputs B,D,E and a single AND gate. In order to decide which outputs (maxterms) should be ANDed together, the function needs to be represented in the maxterm canonical form, i.e.

$$G(B,D,E) = (B+D'+E')(B'+E) = (B+D'+E')(B'+D'+E)(B'+D+E) = \Pi M(3,4,6)$$

In order to generate the required function $F(A,B,C,D,E) = (A+B+C+E') G(B,D,E)$, the additional product term is fed to Enable (EN) input as $EN' = (A+B+C+E') = (A'B'C'E)'$. This requires a second AND gate.

Grading: due to a typo in the original K-map specification for this problem, implementation of the Boolean function $F(A,B,C,D,E)$ requires two AND gates rather than one. So full credit (for this problem) will be given to students who showed correct algebraic/analytic representation of $F(A,B,C,D,E)$, in either min POS or SOP form, - this corresponds, roughly, to Part (1) in the above solution.

(b) For the original counter (with negative edge-triggered flip-flops):

Flip-Flop operation table

- Q₁ complemented on negative edge of CP
- Q₂ complemented if [Q₈=0 and Q₁: 1→0]
- Q₂ cleared if [Q₈=1 and Q₁: 1→0]
- Q₄ complemented if [Q₂: 1→0]
- Q₈ complemented if [Q₄Q₂=11 and Q₁: 1→0]
- Q₈ cleared if [(Q₄ =0 or Q₂=0) and Q₁: 1→0]

These conditions result in the following count sequence, starting from initial state 0000
This is a BCD or modulo 10 counter 0,1,2,...,9 and repeat.

	Q ₈	Q ₄	Q ₂	Q ₁
→	0	0	0	0
	0	0	0	1
	0	0	0	0
	0	0	1	0
	0	0	1	1
	0	0	1	0
	0	0	0	0
	0	1	0	0
	0	1	0	1
	0	1	0	0
	0	1	1	0
	0	1	1	1
	0	1	1	0
	1	1	0	0
	1	0	0	0
	1	0	0	1
	1	0	0	0

Transition states are bold and italicized

ANALYSIS of UNUSED STATES

Present Q₈Q₄Q₂Q₁: 1010 1011 1100 1101 1110 1111

Next state : 1011 0100 1101 0100 1111 0000

→ So this counter is self-starting.

For the counter with positive edge-triggered flip-flops:

Flip-Flop operation table

Q_1 complemented on positive edge of CP

Q_2 complemented if [$Q_8=0$ and $Q_1: 0 \rightarrow 1$]

Q_2 cleared if [$Q_8=1$ and $Q_1: 0 \rightarrow 1$]

Q_4 complemented if [$Q_2: 0 \rightarrow 1$]

Q_8 complemented if [$Q_4Q_2=11$ and $Q_1: 0 \rightarrow 1$]

Q_8 cleared if [$(Q_4=0$ or $Q_2=0)$ and $Q_1: 0 \rightarrow 1$]

These conditions result in the following count sequence, assuming initial state 0000.

Q_8	Q_4	Q_2	Q_1	State
0	0	0	0	0
0	0	0	1	
0	0	1	1	
0	1	1	1	7
0	1	1	0	6
0	1	1	1	
1	1	0	1	13
1	1	0	0	12
1	1	0	1	
0	1	0	1	5
0	1	0	0	4
0	1	0	1	
0	1	1	1	
0	0	1	1	3
0	0	1	0	2
0	0	1	1	
0	0	0	1	1

Transition states are bold and italicized

This counter also cycles through a sequence of 10 states: 0, 7, 6, 13, 12, 5, 4, 3, 2, 1, and repeat.