

**Problem 9 (a)** A buck converter is to be designed to deliver power from a DC input with voltage 12 V to an output of 5 V. The switching frequency is chosen to be  $f = 25$  kHz. The specifications call for a 20 mV peak-to-peak output-voltage ripple, and a 0.8 A peak-to-peak inductor-current ripple. Assume all switching and filter components are ideal. **2 points**

- (i) What is the duty cycle that the converter should operate at?
- (ii) What value of filter inductance would meet the specifications?
- (iii) What value of filter capacitance would meet the specifications?
- (iv) Assuming a load resistance,  $R = 500\ \Omega$ , what is the critical filter inductance for the converter? (Recall, the converter operates at the boundary of continuous- and discontinuous-current conduction modes when the inductance is chosen to be the *critical filter inductance*.)

**Problem 9 (b)** Consider a power system composed of two buses. Bus#1 is connected to a generator, and bus#2 is a load bus. The load consumes 1 p.u. active and 0.5 p.u. reactive power, and it is connected to the generator through a transmission line with impedance  $Z_{\text{line}} = 0.02 + j0.06$  pu. Also, there is a capacitor for power factor correction connected to the load bus with admittance  $Y_{\text{cap}} = j0.25$  pu. The terminal voltage of the generator is  $V_1 \angle \theta_1 = 1 \angle 0$  pu.      **2 points**

- (i) Draw a one-line diagram of the power system described above and write out the admittance matrix of the network.
- (ii) Write the power flow equations that you would have to solve numerically to compute the load-bus voltage magnitude and angle, i.e.,  $V_2 \angle \theta_2$ . **[YOU DO NOT HAVE TO SOLVE THESE EQUATIONS]**