

Problem 9 (a) A buck converter is to be designed to deliver power from a DC input with voltage 12 V to an output of 5 V. The switching frequency is chosen to be $f = 25$ kHz. The specifications call for a 20 mV peak-to-peak output-voltage ripple, and a 0.8 A peak-to-peak inductor-current ripple. Assume all switching and filter components are ideal.

- (i) What is the duty cycle that the converter should operate at?
- (ii) What value of filter inductance would meet the specifications?
- (iii) What value of filter capacitance would meet the specifications?
- (iv) Assuming a load resistance, $R = 500 \Omega$, what is the critical filter inductance for the converter? (Recall, the converter operates at the boundary of continuous- and discontinuous-current conduction modes when the inductance is chosen to be the *critical filter inductance*.)

Solution 9 (a)

- (i) The input voltage, $V_{\text{in}} = 12$ V; and output voltage, $V_{\text{out}} = 5$ V. The duty cycle, D , is given by

$$D = \frac{V_{\text{out}}}{V_{\text{in}}} = \frac{5}{12} \approx 41.67\%. \quad (1)$$

- (ii) With the active switch turned on, we can write

$$V_{\text{in}} - V_{\text{out}} = L \frac{di}{dt}, \quad (2)$$

where i denotes the instantaneous inductor current. With a straight-line approximation for the inductor current, we get

$$V_{\text{in}} - V_{\text{out}} \approx L \frac{\Delta i}{DT}, \quad (3)$$

where $T = f^{-1}$ is the switching period and Δi is the current ripple. Substituting the specifications of the converter and the duty cycle from (1),

$$L = \frac{(V_{\text{in}} - V_{\text{out}})D}{\Delta i \cdot f} = \frac{(12 - 5)5}{12 \times 0.8 \times 25 \times 10^3} \approx 146 \mu\text{H}. \quad (4)$$

- (iii) The instantaneous capacitor current is given by

$$i = C \frac{dv}{dt} \quad (5)$$

Since the average capacitor current is zero, assuming the inductor ripple current is completely absorbed by the capacitor, we can write

$$\int_{i_{\text{ripple}} > 0} i_{\text{ripple}} dt = \frac{1}{2} \times \frac{T}{2} \times \frac{\Delta i}{2} = C \Delta v \quad (6)$$

Substituting the values of the allowed current ripple Δi and the allowed voltage ripple Δv , we get

$$C = \frac{T \times \Delta i}{8 \times \Delta v} = \frac{0.8}{8 \times 25 \times 10^3 \times 20 \times 10^{-3}} = 200 \mu\text{F}. \quad (7)$$

- (iv) Denote the *critical inductance* of the dc-dc buck converter by L_{crit} . Recall that the critical inductance is the minimum inductance required to avoid discontinuous conduction mode (DCM) under all operating conditions. That is, if the chosen inductor for the dc-dc buck converter, $L > L_{\text{crit}}$, then DCM is avoided. On the other hand, if the dc-dc buck converter inductor $L < L_{\text{crit}}$, then the converter always operates in DCM. For $L = L_{\text{crit}}$, $\Delta i = 2I_{\text{out}}$, where $I_{\text{out}} = V_{\text{out}}/R$ is the average output current. With this operating mode in mind, we get

$$L_{\text{crit}} = \frac{(V_{\text{in}} - V_{\text{out}})D}{\Delta i \cdot f} = \frac{(V_{\text{in}} - V_{\text{out}})D}{2I_{\text{out}} \cdot f} = \frac{(12 - 5)5}{12 \times 2(5/500) \times 25 \times 10^3} \approx 5.83 \text{ mH}. \quad (8)$$