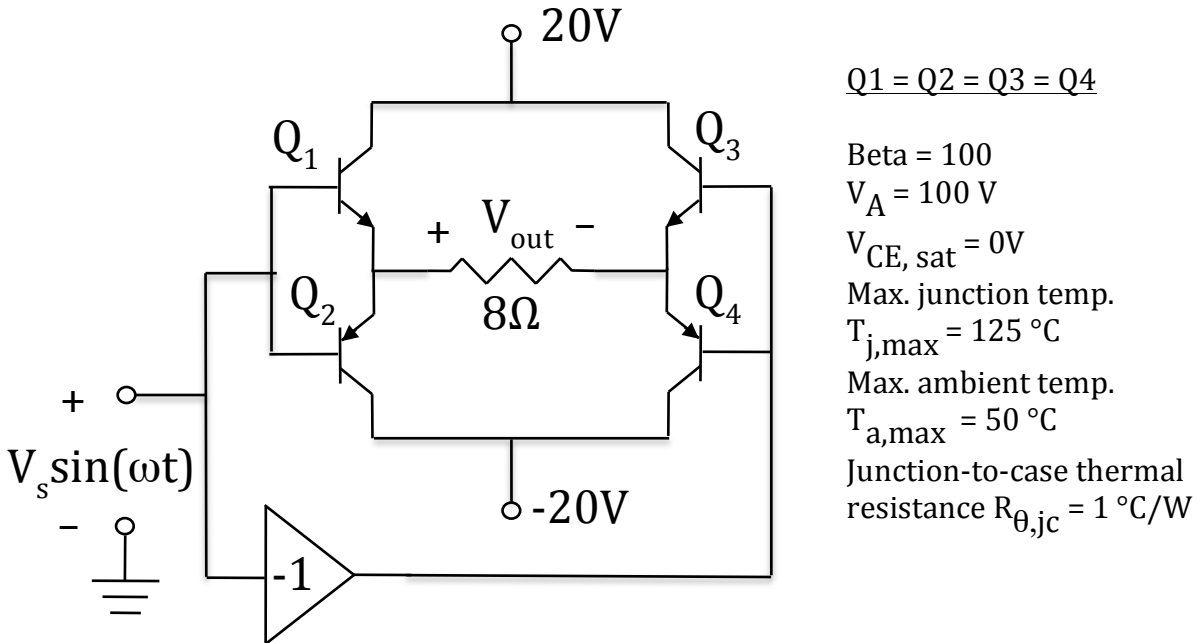


The amplifier shown below is termed a bridge amplifier. The amplifier symbol with the -1 inside is an inverting amplifier with unity gain. The BJT characteristics are shown next to the circuit diagram.



1. (0.5 points)  
Estimate the maximum average power the circuit can deliver to the 8 ohm load.
2. (1 point)  
What is the efficiency ( $\langle P_{\text{load}} \rangle / \langle P_{\text{supplies}} \rangle$ ) at maximum output signal swing?
3. (0.5 points)  
What should be the peak voltage rating and current rating of the transistors. Include a 50% factor of safety.
4. (1 point)  
What is the maximum average power dissipated in a transistor?
5. (1 point)  
The transistors are mounted next to each other on a common heat sink. Specify the required heat sink thermal resistance so that  $T_{j, \text{max}}$  is not exceeded when the ambient is at  $50^\circ\text{C}$ .