

1)  $M1, M2: I_D = 25 \mu A$

$$I_D = \frac{\mu_p C_{ox}}{2} \left(\frac{W}{L}\right)_1 V_{ov}^2$$

$$V_{ov} = \sqrt{\frac{2 I_D}{\mu_p C_{ox} (W/L)_1}}$$

$$= \sqrt{\frac{2(25 \times 10^{-6})}{60 \times 10^{-6} (100)}} = 0.091 V$$

2) Total voltage required to keep  $M1$  in active is

$$V_{ov} = 0.091 V$$

Total voltage across diode connected  $M2$  is

$$V_t + 2V_{ov} = 0.5 + 2(0.091) = 0.683 V$$

$$10 \mu A = \frac{\mu_p C_{ox}}{2} \left(\frac{W}{L}\right)_2 (2V_{ov})^2$$

$$\left(\frac{W}{L}\right)_2 = \frac{10(2)}{60} \frac{1}{(2(0.091))^2} = 10$$

=

$$3) \quad A_v = G_m R_o$$

$$G_m = g_{m1,2} = \sqrt{2I_{D1,MP} \left( \frac{W}{L} \right)} = \cancel{5.48} 5.48 \times 10^{-4} \text{ S}$$

$$R_o = r_{oDP} \parallel r_{oMir}$$

$r_{oDP}$ :

$$r_{o2} = r_{o2A} = \frac{8}{25 \times 10^{-6}} = \cancel{32k} 320 \text{ k}\Omega$$

answer is same as source degenerated CS amplifier

$$\begin{aligned} r_{oDP} &= r_{o2A} (1 + g_{m2} r_{o2}) + r_{o2} \\ &= 32 \times 10^4 (1 + 5.48 \times 10^{-4} (32 \times 10^4)) + 32 \times 10^4 \\ &= \cancel{32 \times 10^3 (18)} + \cancel{32 \times 10^3} \\ &= \cancel{596000 \Omega} 56 \text{ M}\Omega \end{aligned}$$

$r_{oMir}$ :

Since transistors match, answer is same as diff pair

$$R_o = \frac{56 \times 10^6}{2} = 28.4 \text{ M}\Omega$$

$$\cancel{R_o = \frac{596,000}{2} = 298,000 \Omega}$$

$$\cancel{A_v = G_m R_o = 5.48 \times 10^{-4} (298,000) = 163}$$

$$\begin{aligned} A_v = G_m R_o &= 5.48 \times 10^{-4} (28 \times 10^6) = \\ &= 15,550 \text{ (93 dB)} \end{aligned}$$