

DIGITAL DESIGN PROBLEM**Problem 1 [0.5 points]**

Implement a magnitude comparator circuit which compares two-bit binary numbers $A=A_1A_0$ and $B=B_1B_0$, and provides 3 outputs ($A>B$, $A=B$, $A<B$), using three 8-to-1 multiplexers and no additional gates.

Solution:

There could be many different solutions to this problem. Suppose A_1 , A_0 , and B_1 are the select inputs to all three 8-to-1 multiplexers, we can have the following true table.


A_1	A_0	B_1	$A = B$	$A > B$	$A < B$
0	0	0	B_0'	0	B_0
0	0	1	0	0	1
0	1	0	B_0	B_0'	0
0	1	1	0	0	1
1	0	0	0	1	0
1	0	1	B_0'	0	B_0
1	1	0	0	1	0
1	1	1	B_0	B_0'	0

Implementation of this truth table is straightforward. The columns under $A=B$, $A>B$, $A<B$ represent the inputs to each 8-to-1 mux starting from the 000 input to the 111 input. For example, $A=B$ is the output of the mux with $I_0=B_0'$, $I_1=0$, $I_2=B_0$, $I_3=0$, $I_4=0$, $I_5=B_0'$, $I_6=0$, $I_7=B_0$.

Problem 2 [1.5 points]

A 4-input priority encoder with enable is shown below. When EI is 0, all outputs are 0. When EI is 1,

 - i) and all 4 x_i inputs are 0, EO is 1 and $y_1=y_0=0$
- ii) and not all 4 x_i inputs are 0, EO is 0 and y_1 and y_0 are the binary encoding for the highest priority x_i input that is 1 (For example, x_3 is highest priority whose binary encoding is 11. x_1 is lowest priority with binary encoding 01 and so on).



(a) [0.4 points] Draw a two-level NAND-gate implementation of this priority encoder. Assume both true and complementary inputs are available.

(b) [0.4 points] Draw a two-level NOR-gate implementation of this priority encoder. Assume both true and complementary inputs are available.

(c) [0.7 points] Draw a diagram of an 8-input priority encoder of the same type using two 4-input priority encoders and a few logic gates.

Solutions:

The truth table for this encoder is

EI	x_3	x_2	x_1	x_0	EO	y_1	y_0
0	-	-	-	-	0	0	0
1	0	0	0	0	1	0	0
1	1	-	-	-	0	1	1
1	0	1	-	-	0	1	0
1	0	0	1	-	0	0	1
1	0	0	0	1	0	0	0

(a) $EO = EI x_3' x_2' x_1' x_0'$
 $y_1 = EI x_3 + EI x_2$
 $y_0 = EI x_3 + EI x_2' x_1$
 Two 2-input NANDs, one 3-input NAND, one 5-input NAND, and one inverter

(b) $EO = (EI' + x_3 + x_2 + x_1 + x_0)'$
 $y_1 = EI (x_3 + x_2)$
 $y_0 = EI (x_3 + x_2')(x_3 + x_1)$
 Four 2-input NORs, one 3-input NORs, one 5-input NOR, and one inverter

(c) This requires two of the 4-input priority encoders, with EO of the higher priority encoder connected to EI of the lower priority encoder, and two 2 input OR gates to OR the y1 and y0 outputs of the two priority encoders.

Problem 3 [2.0 points]

(a) [0.5 points] A basic lawn sprinkler system waters the lawn at 8am, once every 3 days. Its operation can be modeled as a Moore-style finite state machine, where a clock period is one day, and a binary output W indicates whether the sprinkler is activated ($W=1$) or not ($W=0$) on that day. Show the transition diagram for this sprinkler control system.

(b) [0.5 points] An advanced sprinkler system has a rain sensor. The presence of rain during a particular day is indicated by the binary input R (with values 0/1 indicating No/Yes_rain). This sprinkler waters the lawn once every 3 days, assuming there has been no rain during previous 2 days. Show the transition diagram (Moore-style) for this advanced sprinkler system.

(c) [1.0 points] Implement the transition diagram of a sprinkler system in part (b) using a 4-bit counter with parallel load capability and external gates. The counter is specified by its operation table shown below. Use the most appropriate state assignment for this counter implementation. (*Implementation* means showing the block diagram with clearly labeled inputs/outputs, and derivation of the Boolean equations for control/data inputs of the counter).


Counter operation table:

(All functions are synchronous with a clock)


<i>Clear</i>	<i>Load</i>	<i>Coun</i> <i>t</i>	<i>Function</i>
0	X	X	Clear
1	0	0	No change
1	1	X	Load
1	0	1	Count up

Solutions:

(a)

 

(b)

 

(c) Use two least significant bits of the counter q_1q_2 to encode 3 states. From the transition diagram: transitions $S_0 \rightarrow S_1$ and $S_1 \rightarrow S_2$ can be implemented via counting function. All other transitions (to state $S_0 \sim 00$) are implemented using CLEAR function. So, we use this state assignment $S_0 \sim 00, S_1 \sim 01, S_2 \sim 10$. Count up function requires $Load=0, Count=1$. Clear input should be zero whenever input $R=1$ or when the system is in state $S_2 (q_1=1)$.

Hence, $Clear = (q_1 + R)' = q_1'R'$
 $Count = 1, Load = 0$, parallel Load inputs are don't cares.

Alternatively, you can use a state transition table.

q_1	q_2	R	q_1^+	q_2^+		Clear	Load	Count
0	0	0	0	1	count	1	0	1
0	0	1	0	0	clear	0	x	x
0	1	0	1	0	count	1	0	1
0	1	1	0	0	clear	0	x	x
1	0	0	0	0	clear	0	x	x
1	0	1	0	0	clear	0	x	x
1	1	0	x	x	x	x	x	x
1	1	1	x	x	x	x	x	x

$Clear = q_1'R'$ or $(q_1+R)'$

$q_1q_2 \backslash R$	00	01	11	10
0	1	1	x	0
1	0	0	x	0

$Load=0$

$q_1q_2 \backslash R$	00	01	11	10
0	0	0	x	x
1	x	x	x	x

$Count= 1$ (clearly seen from the truth table).