

a)
12 pt

A	B	C	D	F
0	0	0	0	0
0	0	0	1	0
0	0	1	0	0
0	0	1	1	1
0	1	0	0	0
0	1	0	1	1
0	1	1	0	0
0	1	1	1	1
1	0	0	0	0
1	0	0	1	1
1	0	1	0	0
1	0	1	1	1
1	1	0	0	0
1	1	0	1	1
1	1	1	0	0
1	1	1	1	1

dad has a "no" veto power, not a "yes" veto.

← tie

← tie

← tie

← tie, dad wins


← veto

b)
0.1 pt

$$\bar{A}\bar{B}CD + \bar{A}B\bar{C}D + \bar{A}BCD + A\bar{B}\bar{C}D + A\bar{B}CD + AB\bar{C}D + ABCD$$



~~logic diagram not drawn~~

c) 0.7 pt

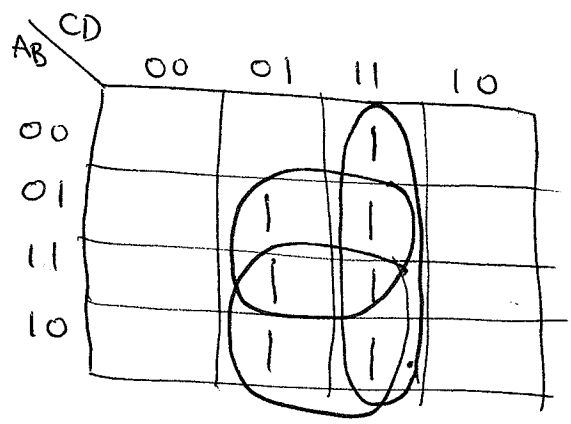


$F = CD + BD + AD$

d) 0.3 pt

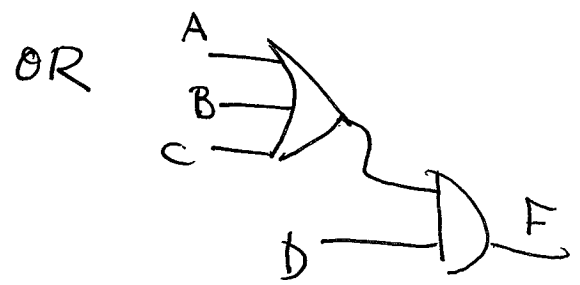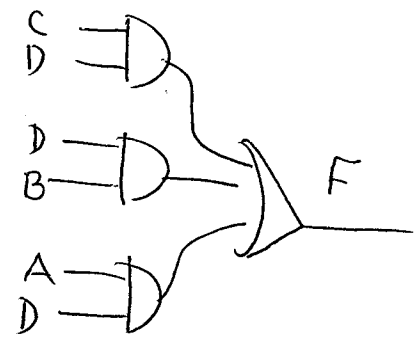


e) 0.2 pt

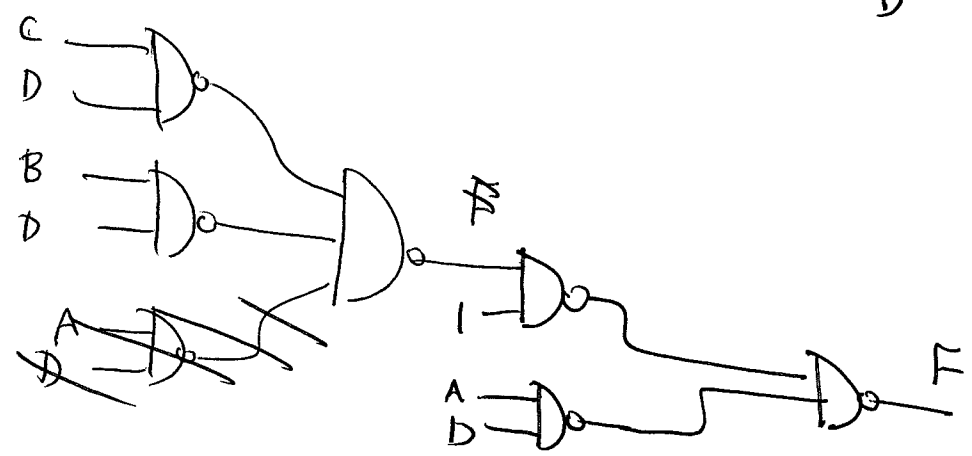

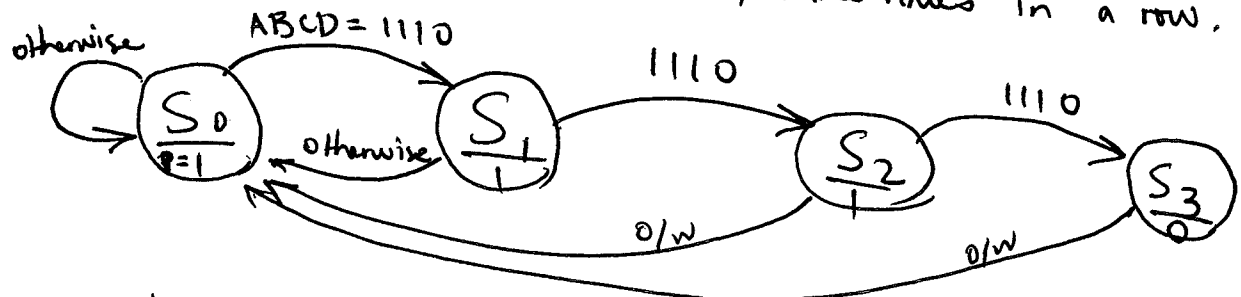f) 1 pt


There are four cases: the father has not vetoed yet, he has vetoed once, twice, three times in a row.



otherwise (or o/w) means $ABCD \neq 1110$

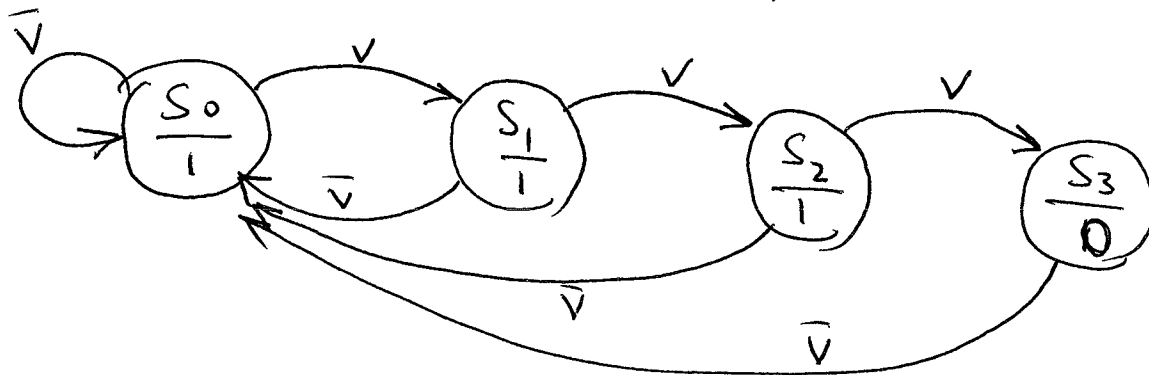g) $S_0 = 00$ $S_1 = 01$ $S_2 = 10$ $S_3 = 11$
 (1.5 pt)

We define an intermediate function $v = ABC\bar{D}$, which is one if a veto was used.



The state machine is essentially a counter w/ reset.

JK excitation table

cur state	→ next state	J K	J	K	Q ⁺
0	→ 0	0X	0	0	Q
0	→ 1	1X	0	1	Q
1	→ 0	X1	1	0	Q
1	→ 1	X0	1	1	Q

cur state	next state v=0	state v=1
S ₀	S ₀	S ₁
S ₁	S ₀	S ₂
S ₂	S ₀	S ₃
S ₃	S ₀	S ₀

cur state (a ₁ a ₂)	next state (Q ₁ Q ₂)	
	v=0	v=1
00	00	01
01	00	10
10	00	11
11	00	00

g) (cont'd)

cur state (Q ₁ , Q ₂)	J ₁ k ₁		J ₂ k ₂	
	v=0	v=1	v=0	v=1
00	0X	0X	0X	1X
01	0X	1X	X1	X1
10	X1	X0	0X	1X
11	X1	X1	X1	X1

J₁

v	Q ₁ , Q ₂			
	00	01	11	10
0	0	0	X	X
1	0	1	X	X

$J_1 = vQ_2$

k₁

v	Q ₁ , Q ₂			
	00	01	11	10
0	X	X	1	1
1	X	X	1	0

$k_1 = Q_2 + \bar{v}$

J₂

v	Q ₁ , Q ₂			
	00	01	11	10
0	0	X	X	0
1	1	X	X	1

$J_2 = v$

k₂

v	Q ₁ , Q ₂			
	00	01	11	10
0	X	1	1	X
1	X	1	1	X

$k_2 = 1$

State output (whether to allow the father to veto)

$\hat{is} = \bar{Q}_1 + \bar{Q}_2$