


Problem #4 Solutions - Electronics

Fall 2012 WPE

- ① Assume loop gain $AB \gg 1$. Check assumption in later problems.

$$A_F = \frac{V_o}{V_s} \approx \frac{1}{\beta}; \quad \beta = \frac{1k}{100k} = 10^{-2}$$

$$A_F \approx 100$$

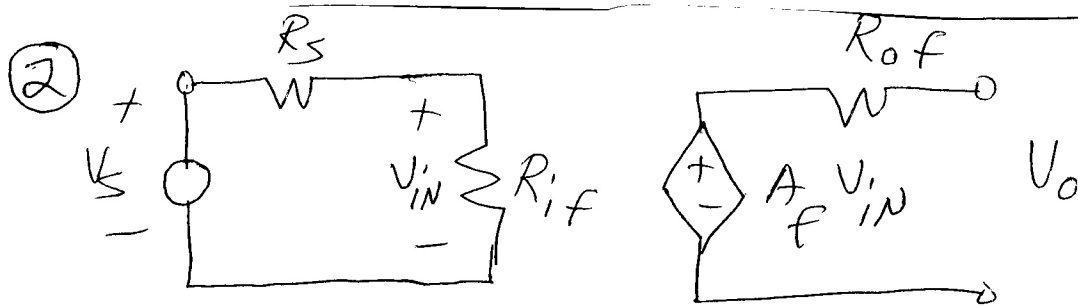

$$V_o = \frac{A_F R_{if}}{(R_s + R_{if})} V_s$$


$$\frac{V_o}{V_s} \geq 0.9 A_F$$

$$\therefore \frac{R_{if}}{R_{if} + R_s} \geq 0.9$$


$$R_s \leq \frac{R_{if}}{9}$$

Need R_{if} value

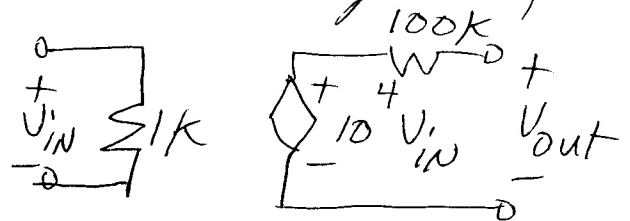
Find R_{if} value
Model open loop amplifier as a voltage amplifier



Loading of feedback circuit

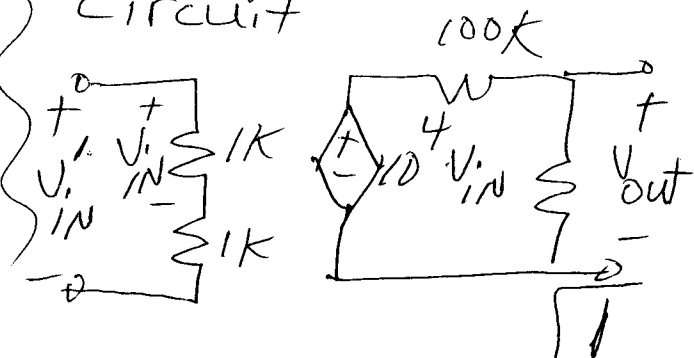

Prob. #4 Solutions Fall 2012 WPE

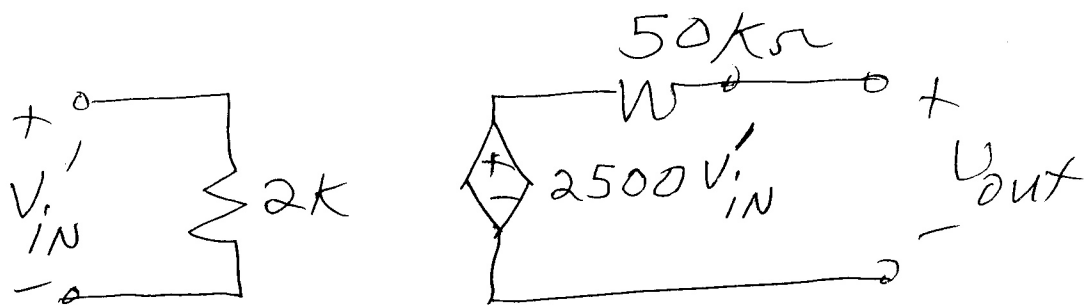

$$R_{if} = R_i' (1 + A_v' \beta) = (2k) \left[1 + [2500] [10^{-2}] \right]$$

$$= (2 \times 10^3) (26) = 52k\Omega$$

$$R_S \leq \frac{52k}{9} = 5.8k\Omega$$

loop gain
= 25
25 \gg 1
prob. #1
assumption
justified



$$\frac{V_O}{V_S} = \frac{R_L}{R_L + R_{of}} \quad 100 \geq 90$$

$$R_{of} = \frac{R_o}{[1 + A_v' \beta]}$$

$$R_L \geq .9R_L + .9R_{of}$$

$$R_L \geq 9R_{of}$$

$$R_L > (9)(1.92k\Omega)$$

$$R_L \geq 17.3k\Omega$$

$$A_v' \beta = 25 \text{ from prob. #2}$$


$$R_{of} = \frac{50k}{26} = 1.92k\Omega$$

Problem #4 Solutions

Electronics - Fall 2012 WPE

If feedback circuit loading effects are ignored then the results for problems # 2 & #3 would be as follows.

Open loop amplifier equiv. ckt

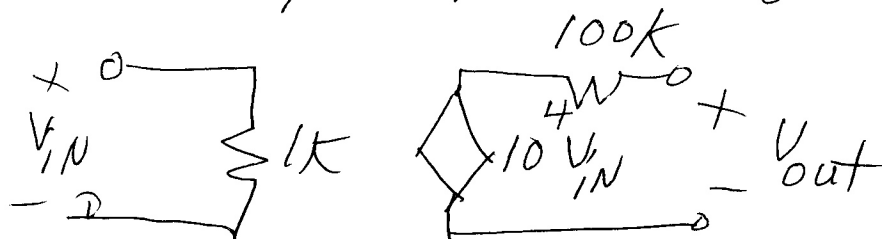

$$R_{if} = (10^3)(1 + 10 \times 10^{-2}) = 100k\Omega$$

$$R_s < \frac{100k}{9} = 11.1k\Omega$$

$$R_{of} = \frac{100k}{100} = 1k$$

$$R_L \geq 9k$$

Ignoring loading of feedback circuit causes about a factor of two error

in #2 & #3 3