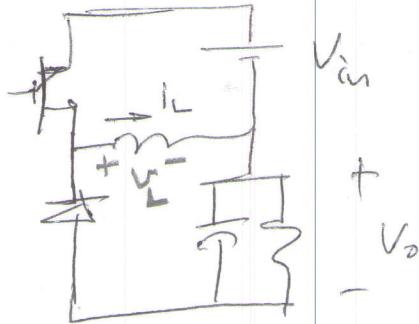


Solution 9A

Spring 2013

1/2



$$V_{in} = 30V, \quad V_o = 60V, \quad f_s = 200\text{ kHz}$$

$$P_{o,\max} = 180W. \quad T_s = \frac{1}{200} = 5\mu s$$

⑨

at the border of Cont./Discant. mode -

$$P_o = \frac{1}{3} P_{o,\max} = \frac{180}{3} = 60W.$$

$$\frac{V_o}{V_{in}} = \frac{D}{1-D} = \frac{60}{30} = 2$$

$$\therefore 2 - 2D = D \quad \text{or} \quad D = \frac{2}{3} = 0.667$$


$$\text{or } 3D = 2$$

$$I_{in} = \frac{P_o (= P_{in})}{V_{in}} = \frac{60}{30} = 2A$$

$$I_o = \frac{P_o}{V_o} = \frac{60}{60} = 1A$$

$$\therefore I_L = I_{in} + I_o = 3A$$

$$I_L = 2 \times I_L = 6A$$

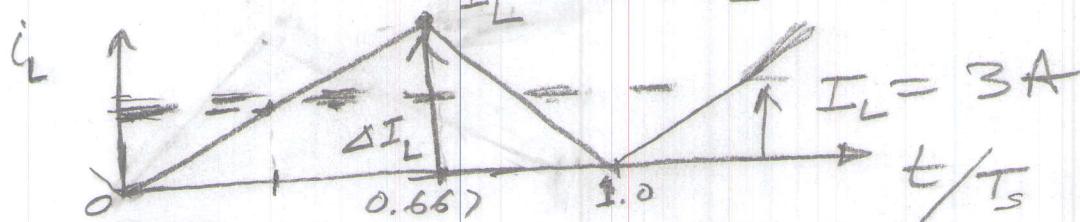


$$\text{During } 0 < t < DT_s \quad V_L = V_{in} = 30V$$

$$\therefore L_{crit} \frac{\Delta I}{\Delta T} = V_{in} \Rightarrow L_{crit} = \frac{30 \times 0.667 \times 5 \mu s}{6A} = 16.667 \mu H$$

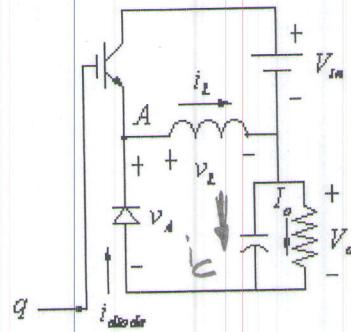
Problem 9A) Power Electronics (2 pts)

A Buck-Boost converter shown below is designed to operate with $V_{in} = 30V$, $V_o = 60V$ and $f_s = 200\text{ kHz}$. The maximum output power level of this converter is $P_{o,\max} = 180W$. Assume ideal components.




(a) (1 pt) It is to be designed such that if the output power is equal to or higher than one-third of $P_{o,\max}$, it remains in the continuous-current conduction mode; below this output power level, it goes into the discontinuous-conduction mode. Calculate the value of the inductor L to satisfy this design condition.

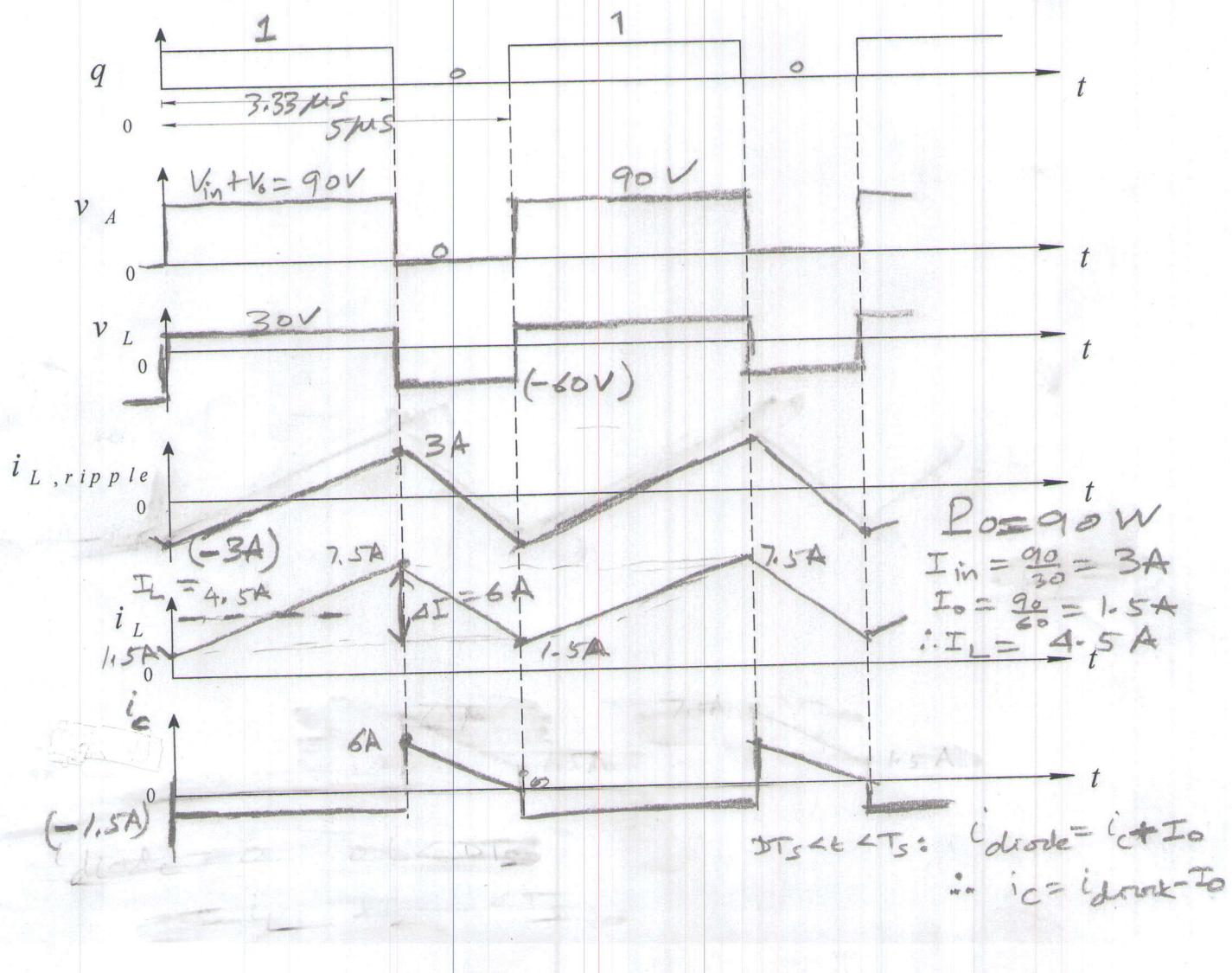(b) (1 pt) This converter is operating at $P_o = 90W$. Calculate and draw the waveforms of the following variables as a function of time in the figure below, labeling both axes as appropriate: v_A , v_L , $i_{L,ripple}$, i_L and i_{diode} . (Note: $i_{L,ripple} = i_L - I_L$).



Problem 9 B) Power Systems

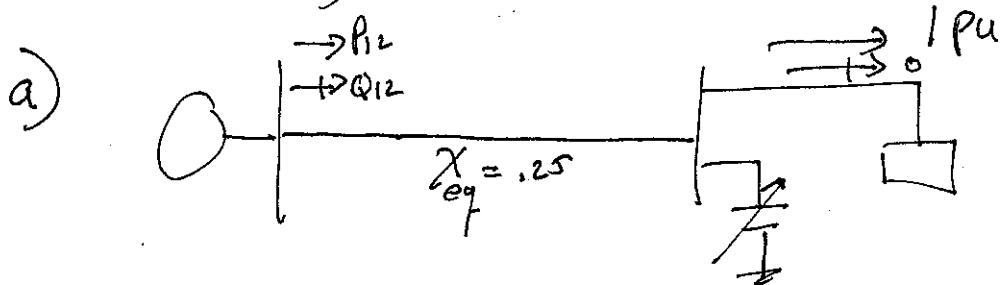

$$\begin{aligned}
 P_{12} + jQ_{12} &= V_1[\theta_1] \left[I_{12} \right]^* = V_1[\theta_1] \left[\frac{V_1[\theta_1] - V_2[\theta_2]}{.25j} \right]^* \\
 &= 1 \left[1 - \left(\frac{1 \cos \theta_2 + j 1 \sin \theta_2}{.25j} \right) \right]^* \\
 &= \left[\frac{(1 - 1 \cos \theta_2) - j 1 \sin \theta_2}{.25j} \right]^* \\
 &= \frac{(1 - \cos \theta_2) + j \sin \theta_2}{-.25j} \\
 &= \frac{(4 - 4 \cos \theta_2) + j 4 \sin \theta_2}{-j} \\
 &= j(4 - 4 \cos \theta_2) - 4 \sin \theta_2
 \end{aligned}$$

$$P_{12} = 1 = -4 \sin \theta_2, \quad \sin \theta_2 = -\frac{1}{4}, \quad \theta_2 = -14.4725^\circ$$

Solu 9B - P₂ 2

Part b)

$$Q_{12} = 4 - 4 \cos \theta_2 = 4 - 4(0.9682) = .1270 \text{ pu}$$

max

Q supplied by SRC:

$$P_{21} + jQ_{21} = V_2[\theta_2] [I_{21}]^*$$

$$= V_2[\theta_2] \left[\frac{V_2[\theta_2] - V_1[\theta_1]}{.25j} \right]^*$$

$$= V_2[\theta_2] \left[\frac{V_2[-\theta_2 - 1]}{-0.25j} \right]$$

$$\underline{\underline{= |V_2|^2 - |V_2| |\theta_2|}}$$


$$= \frac{1 - (\cos \theta_2 + j \sin \theta_2)}{-.25j} = \frac{(4 - 4 \cos \theta_2) - j 4 \sin \theta_2}{-j}$$

$$= j(4 - 4 \cos \theta_2) + 4 \sin \theta_2$$

$$P_{21} = 4 \left(\sin(-14.725^\circ) \right) = -1$$

$$Q_{21} = +.1270$$

Resulting Power Flow

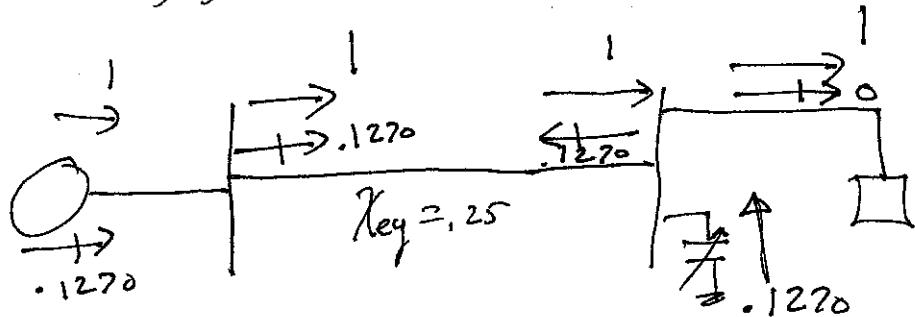

Part c)


One line opened $\chi_{eq} = .5$

$$P_{12} + jQ_{12} = \frac{(1 - \cos \theta_2) + j \sin \theta_2}{-.5j}$$

$$1 + jQ_{12} = j(2 - 2 \cos \theta_2) - 2 \sin \theta_2$$

$$1 = -2 \sin \theta_2 \quad \sin \theta_2 = -.5 \\ \theta_2 = -30^\circ$$

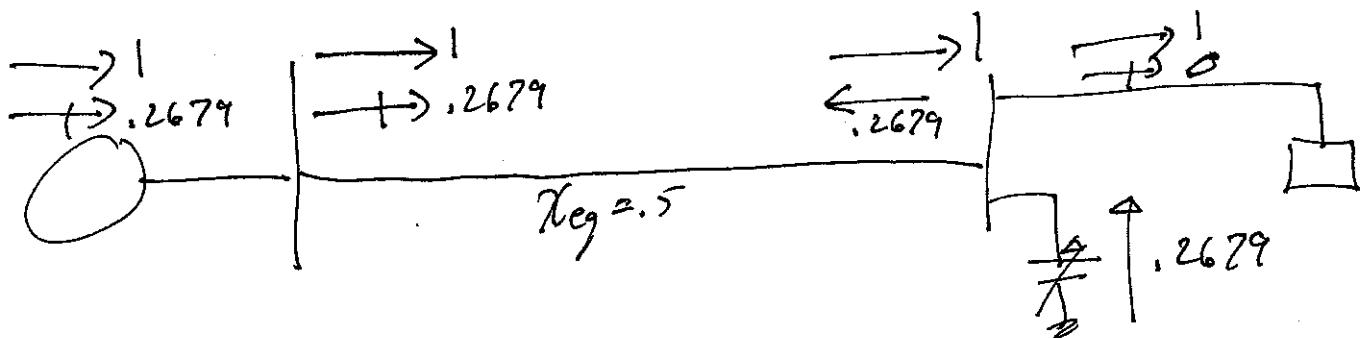
$$Q_{12} = 2 - 2 \cos \theta_2 = 2 - 2 (.866) = .2679$$



Note Q_{gen} is $> Q^{max}$ for generator

Solu Prob 9B Pg 4

d) We want to bring θ_{12} down to 20mrad or .2 pu. The only way is to reduce $|V_1|$ below 1.0

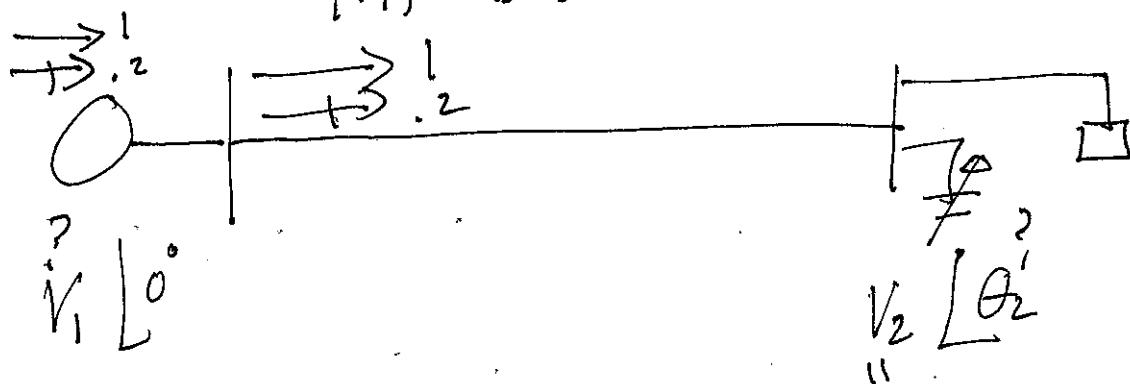

Now $|V_1|$ is unknown, θ_2 is unknown.

assume θ_1 is still zero, V_2 is still 1.0

$$\begin{aligned}
 I_{12j} &= V_1 \angle \theta_1 \left[\frac{|V_1| \angle \theta_1 - |V_2| \angle \theta_2}{-5j} \right]^* \\
 &= |V_1| \left[\frac{|V_1| - (1 \cos \theta_2 + j \sin \theta_2)}{-5j} \right]^* \\
 &= |V_1| \left[\frac{(|V_1| - \cos \theta_2) - j \sin \theta_2}{-5j} \right]^* \\
 &= |V_1| \left[\frac{(|V_1| - \cos \theta_2) + j \sin \theta_2}{-5j} \right] \\
 &= \underline{\frac{(|V_1|^2 - |V_1| \cos \theta_2) + j |V_1| \sin \theta_2}{-5j}}
 \end{aligned}$$

$$1 + .2j = 2j \left(V_1^2 - V_1 \cos \theta_2 \right) - 2 V_1 \sin \theta_2$$

$$1 = -2 V_1 \sin \theta_2 \Rightarrow V_1 \sin \theta_2 = -.5$$

$$.2 = 2 \left(V_1^2 - V_1 \cos \theta_2 \right) \Rightarrow V_1^2 - V_1 \cos \theta_2 = .1$$

$$V_1^2 \sin^2 \theta_2 = .25 \quad V_1^2 \cos^2 \theta_2 = (V_1^2 - .1)^2$$

$$V_1^2 (\sin^2 \theta_2 + \cos^2 \theta_2) = (V_1^2 - .1)^2 + .25$$

$$V_1^2 = V_1^4 - 0.2 V_1^2 + .01 + .25 =$$

$$\text{let } x = V_1^2 \quad x^2 - 1.2x + .26 = 0$$

Using quadratic formula $x = .9162$, $V_1 = .9572$

$$V_1 \sin \theta_2 = -.5$$

$$\sin \theta_2 = -.5 / .9572 = -.5223$$

$$\theta_2 = -31.49^\circ$$

Voltage at gen must be dropped to .9572 pu
to get gen mvar to 20 mvar output.