

# Prob 9A Solution

load 1  $V_{LL} = 440$   $V_{LN} = \frac{440}{\sqrt{3}} \angle 0^\circ = 254.03 \angle 0^\circ$   
assume  $V_{LN}$  at load is at  $0^\circ$

$$I_{\text{line load 1}} = \frac{100000}{V_{LL} \cdot \sqrt{3}} = 131.2 \angle -36.87^\circ$$

$$P_{\text{load 1}} + jQ_{\text{load 1}} = 80 \text{ kW} + j60 \text{ kVAR}$$

load 2

$$I_{\text{line load 2}} = \frac{120000}{V_{LL} \sqrt{3} (0.96)} = 164.02 \angle 16.26^\circ$$

$$P_{\text{load 2}} + jQ_{\text{load 2}} = 120 \text{ kW} + j(-35 \text{ kVAR})$$

$$I_{\text{load total}} = 264.4 \angle -7.12^\circ$$

---

$$V_{LN \text{ highside}} = \frac{4400}{\sqrt{3}} \angle 0^\circ = 2540 \angle 0^\circ$$

$$I_{\text{line high side}} = (1/10) I_{\text{load total}} = 26.4 \angle -7.12^\circ$$

$$\begin{aligned} V_{LN \text{ gen}} &= V_{LN \text{ highside}} + I_{\text{line highside}} \times (2 + j4) \\ &= 2.608 \text{ kV} \angle 2.16^\circ \end{aligned}$$

$$V_{LL \text{ gen}} = 4516 \angle 32^\circ$$


$$A \equiv a$$

$$\bar{V}_{AN} = \frac{V_d}{2} + \bar{V}_{An} = \frac{300}{2} + 112.5 \sin \omega t$$

No negative terminal of the dc-bus

(a) 
$$d_A = \frac{\bar{V}_{AN}}{V_d} = 0.5 + 0.375 \sin \omega t$$

Similarly  $d_B$  &  $d_C$ .

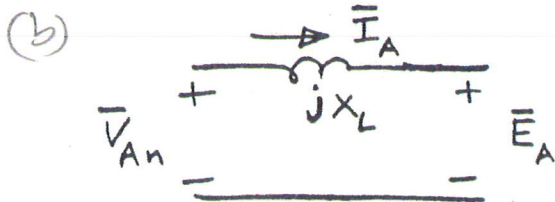

for purposes of drawing phasors, we will advance both voltages by  $90^\circ$  so that

$$\bar{V}_{An}(t) = 112.5 \cos \omega t \quad \checkmark$$

and, 
$$E_A(t) = 106.14 \cos(\omega t - 6.6^\circ) \quad \checkmark$$

$$\therefore \bar{V}_{An} = 112.5 \angle 0^\circ \text{ V}, \quad \bar{E}_A = 106.14 \angle -6.6^\circ \text{ V}$$

$$\bar{V}_{An} = \bar{E}_A + jX_L \bar{I}_A$$

$$X_L = 2\pi f L$$

$$= 2\pi \times 45 \times 5 \times 10^{-3}$$

$$= 1.414 \Omega$$

$$\bar{I}_A = \frac{\bar{V}_{An} - \bar{E}_A}{jX_L}$$

$$= \frac{112.5 \angle 0^\circ - 106.14 \angle -6.6^\circ}{j 1.414} = 9.97 \angle -30.1^\circ \text{ A}$$

$\therefore \bar{I}_A(t) = 9.97 \cos(\omega t - 30.1^\circ)$  but in fact,

$\bar{I}_A(t) = 9.97 \sin(\omega t - 30.1^\circ)$ , taking away the advance by  $90^\circ$ .

Similarly  $\bar{I}_B$  and  $\bar{I}_C(t)$ .

$$\begin{aligned}\bar{i}_{dA}(t) &= d_A(t) \bar{i}_A(t) \\ &= (0.5 + 0.375 \sin \omega_1 t) 9.97 \sin(\omega_1 t - 30.1^\circ) \\ &= 4.985 \sin(\omega_1 t - 30.1^\circ) + 3.74 \sin \omega_1 t \cdot \sin(\omega_1 t - 30.1^\circ)\end{aligned}$$

$$\sin A \cdot \sin B = \frac{1}{2} \{ \cos(A-B) - \cos(A+B) \}$$

$$\begin{aligned}\therefore \bar{i}_{dA} &= 4.985 \sin(\omega_1 t - 30.1^\circ) + 1.87 \cos(30.1^\circ) - 1.87 \cos(2\omega_1 t - 30.1^\circ) \\ &= \underbrace{1.618}_{\text{dc}} + \underbrace{4.985 \sin(\omega_1 t - 30.1^\circ)}_{\text{fund. freq.}} - \underbrace{1.87 \cos(2\omega_1 t - 30.1^\circ)}_{\text{2nd harmonic}}\end{aligned}$$

$$(c) \quad \bar{i}_d = \bar{i}_{dA} + \bar{i}_{dB} + \bar{i}_{dc}$$

The fundamental frequency components in  $\bar{i}_{dA}$ ,  $\bar{i}_{dB}$  and  $\bar{i}_{dc}$  combine to zero. The same happens to the 2nd harmonic components. Therefore,

$$\bar{i}_d = 3 \times 1.618 = 4.854 \text{ A}$$