

1

Problem 4 Soln:

1) $Q_1 - Q_4$ Have $45 \mu A$ drain current

$$g_m = 0.3 \text{ mA/V}^2$$

$$r_o = 222 \text{ k}\Omega$$

$Q_5 - Q_8$ Have $90 \mu A$ drain current

$$g_m = 0.6 \text{ mA/V}^2$$

$$r_o = 111 \text{ k}\Omega$$

$$A_{v1} = -g_{m1} (r_{o2} || r_{o4}) = -0.3 (222 || 222) = -33.3 \text{ V/V}$$

First stage

$$A_{v2} = -g_{m5} (r_{o6} || r_{o7}) = -33.3 \text{ V/V}$$

Second stage

$$\text{Total gain } A_{vT} = 1109 \text{ V/V}$$

2) Out put can go from:

$$-V_{SS} + |V_{ovl}| \leq V_o \leq V_{DD} - |V_{ovl}|$$

$$-2.5 + 0.3 \leq V_o \leq 2.5 - 0.3$$

$$-2.2 \leq V_o \leq 2.2$$

common mode
Input, is more restrictive:

See next page

~~$$-V_{SS} + |V_{ovl}| \leq V_{in} \leq V_{DD} - |V_{ovl}|$$~~

~~$$-V_{SS} + |V_{ovl}| \leq V_{in} \leq V_{DD} - |V_{ovl}|$$~~

2

Problem 4 Soln, cont'd

$$-V_{SS} + V_{tn} + V_{ov} + V_{ov} - |V_{tp}| - V_{ov} \leq V_{in} \leq V_{DD} - |V_{tp}| - V_{ov} - V_{ov}$$

$$-2.5 + 0.7 + 0.3 - 0.8 \leq V_{in} \leq 2.5 - 0.8 - 0.3 - 0.3$$

$$-2.3 \leq V_{in} \leq 1.1V$$

Taking the worse of these limits

$$-2.2V \leq V \leq 1.1V$$

3) Gain of second stage is -33.3
Miller mult. factor is 34.3

$$C_M = ~~8.343~~ 8 \cdot 34.3 \text{ pF} =$$

$$= 2.74 \times 10^{-10} \text{ F}$$

$$\omega_p \approx \frac{1}{(r_{o2} || r_{o4}) C_M} = 3.28 \times 10^4 \text{ r/s}$$

(5 kHz)

4 Slew Rate


$$\frac{dv_c}{dt} = \frac{I_c}{C_c} = \frac{90 \times 10^{-6}}{8 \times 10^{-12}} = 1.13 \times 10^7 \text{ V/s}$$

(11.3 V/ μ s)

Problem 4, cont'd

5

connecting the source follower:

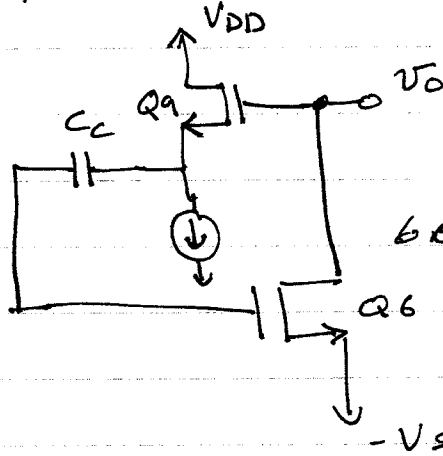

Now v_o has to be greater than
 $-V_{ss} + V_{ov} + V_{th}$
 $= -2.5 + 0.3 + 0.7$
 $-V_{ss} = -1.5$

It further restricts the output making the total follower range:

$$-1.5V \leq V \leq +1.1V$$