

Problem 4 - Analog and Digital Electronics - Solutions

$$a) \quad I_{EQ} = \frac{\beta+1}{\beta} I_{CQ} = 10.1 \mu A$$

$$\therefore R_E = \frac{V_{EQ}}{I_{EQ}} = 990 \Omega$$


$$I_B R_B = \frac{I_{CQ}}{\beta} R_B = 15 - 0.7 - 10 = 4.3$$

$$\therefore R_B = 43 \text{ k}\Omega$$

$$b) \quad r_{\pi} = \frac{\beta V_T}{I_{CQ}} = 260 \Omega$$

$$r_o = \frac{V_A}{I_{CQ}} = 20 \text{ k}\Omega$$

Small Signal Ckt. at midband:

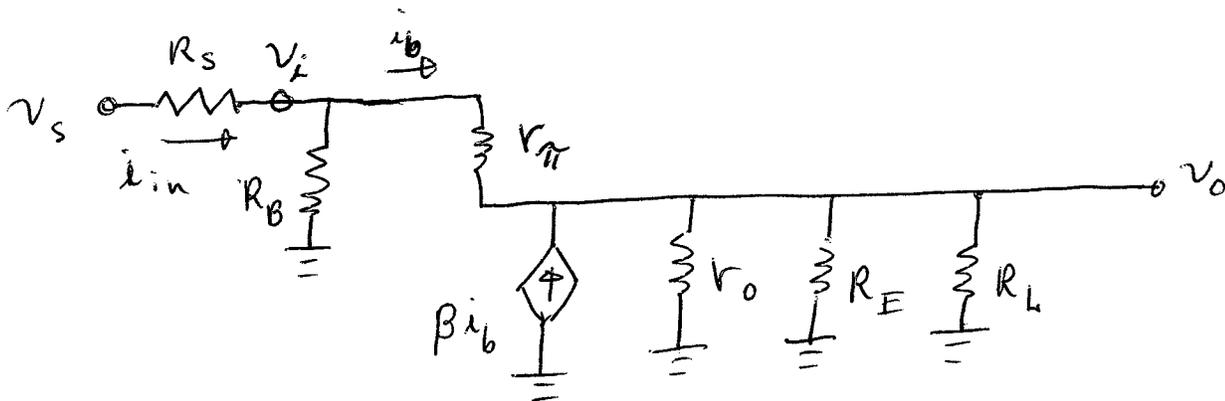

For R_{in} : Let $R_L' = R_L \parallel r_o \parallel R_E = 794 \Omega$

$$i_{in} = \frac{v_i}{R_B} + i_b$$

$$v_i = i_b r_{\pi} + (\beta+1) i_b R_L'$$

$$\therefore i_b = v_i / [r_{\pi} + (\beta+1) R_L']$$

$$\therefore R_{in} = v_i / i_{in} = \frac{1}{1/R_B + 1/[r_{\pi} + (\beta+1) R_L']} = 28 \text{ k}\Omega$$

Problem 4 - Analog and Digital Electronics - Solutions

For R_{out} : Ground V_s and apply V_x to v_o and determine i_x w. R_L .

$$\text{Let } R_E' = R_E \parallel v_o = 943 \Omega$$

$$R_s' = R_s \parallel R_B = 249 \Omega$$

$$\therefore i_x = \frac{V_x}{R_E'} + \frac{V_x}{r_\pi + R_s'} + \beta \frac{V_x}{r_\pi + R_s'}$$

$$\therefore R_{out} = \frac{V_x}{i_x} = \frac{1}{\frac{1}{R_E'} + \frac{1+\beta}{r_\pi + R_s'}} = 5 \Omega$$

For A_v :
$$i_b = \frac{v_i - v_o}{r_\pi}$$

$$v_o = (\beta + 1) i_b R_L' = \frac{(\beta + 1) R_L'}{r_\pi} (v_i - v_o)$$

$$\therefore A_v = \frac{v_o}{v_i} = \frac{(\beta + 1) R_L'}{[r_\pi + (\beta + 1) R_L']} = 0.997$$

For G_v :

$$G_v = \frac{v_o}{v_s} = \frac{v_o}{v_i} \frac{v_i}{v_s} = A_v \frac{R_{in}}{R_{in} + R_s} = 0.988$$

Problem 4 - Analog and Digital Electronics - Solutions


c) i) $f_{bc1} = \frac{1}{2\pi(R_s + R_{in})C_1} = 0.56 \text{ Hz}$

$f_{bc2} = \frac{1}{2\pi(R_{out} + R_L)C_2} = 31.8 \text{ Hz}$

$\therefore f_b \approx 31.8 \text{ Hz}$

ii)

Small signal ckt. at high frequency:

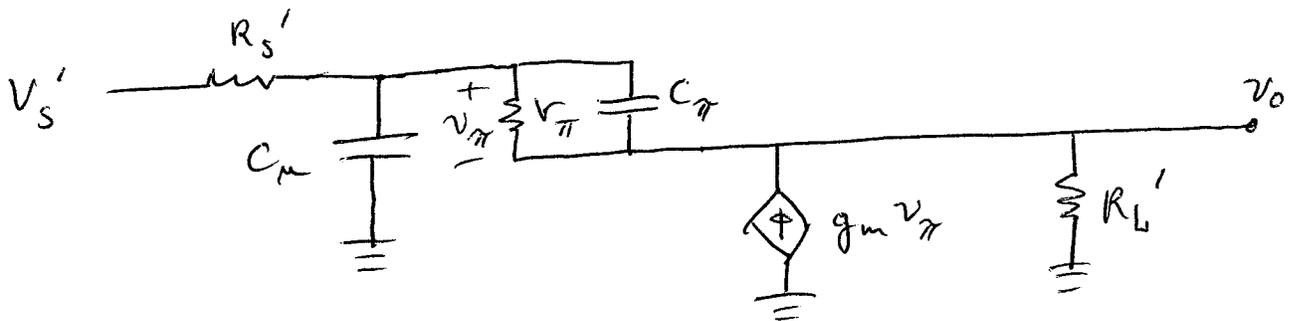


Now Use Miller Effect:

$g_m = \frac{I_{CQ}}{V_T} = 385 \text{ mA/V}$

Now $1 - A_v = 1 / \left[1 + \frac{(1 + \beta)R_L'}{r_\pi} \right] = 1 / 309$

Yields on input side:

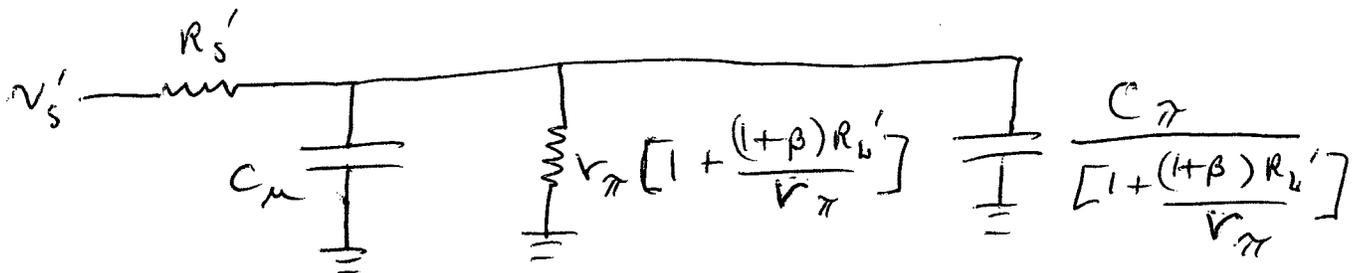

Problem 4 - Analog and Digital Electronics - Solutions

$$\underline{\text{Let:}} \quad C_T = C_\mu + \frac{C_\pi}{\left[1 + \frac{(1+\beta)R_L'}{r_\pi}\right]} = 5 \text{ pF}$$

$$\underline{\text{Let:}} \quad R_T = R_S' \parallel r_\pi \left[1 + \frac{(1+\beta)R_L'}{r_\pi}\right] = 248 \Omega$$

$$\therefore f_H = \frac{1}{2\pi C_T R_T} \approx 128 \text{ MHz}.$$