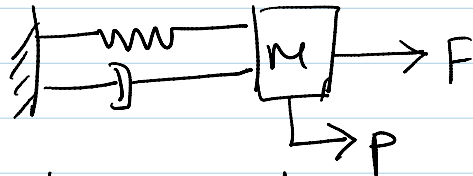


## Lecture 2

Saturday, January 21, 2012  
4:58 PM

Last time:


Consider a spring mass damper system



⊗ The position of the mass is  $p$

⊗ A force  $F$  is applied to the mass  $M$

Free body diagram

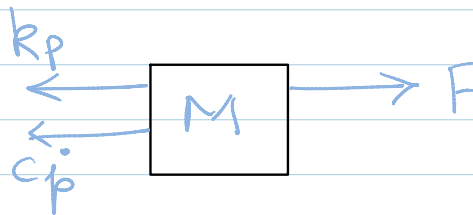

$$M\ddot{p} = F - k_p - c\dot{p}$$

and thus

$$M\ddot{p} + c\dot{p} + k_p = F$$

⊗ Converting into state space

Let

$$x_1 = p$$

$$x_2 = \dot{p}$$


Thus,

$$\begin{aligned} \dot{x}_1 &= \dot{p} = x_2 \\ \dot{x}_2 &= \ddot{p} = -\frac{k}{m}p - \frac{c}{m}\dot{p} + \frac{F}{m} \end{aligned}$$

$$= -\frac{k}{m}x_1 - \frac{c}{m}x_2 + F$$


$$\therefore \dot{x}^0 = \begin{bmatrix} \dot{x}_1^0 \\ \dot{x}_2^0 \end{bmatrix} = \begin{bmatrix} 0 & 1 \\ -\frac{k}{m} & -\frac{c}{m} \end{bmatrix} \begin{bmatrix} x_1 \\ x_2 \end{bmatrix} + \begin{bmatrix} 0 \\ \frac{1}{m} \end{bmatrix} F$$

Analog Circuit:

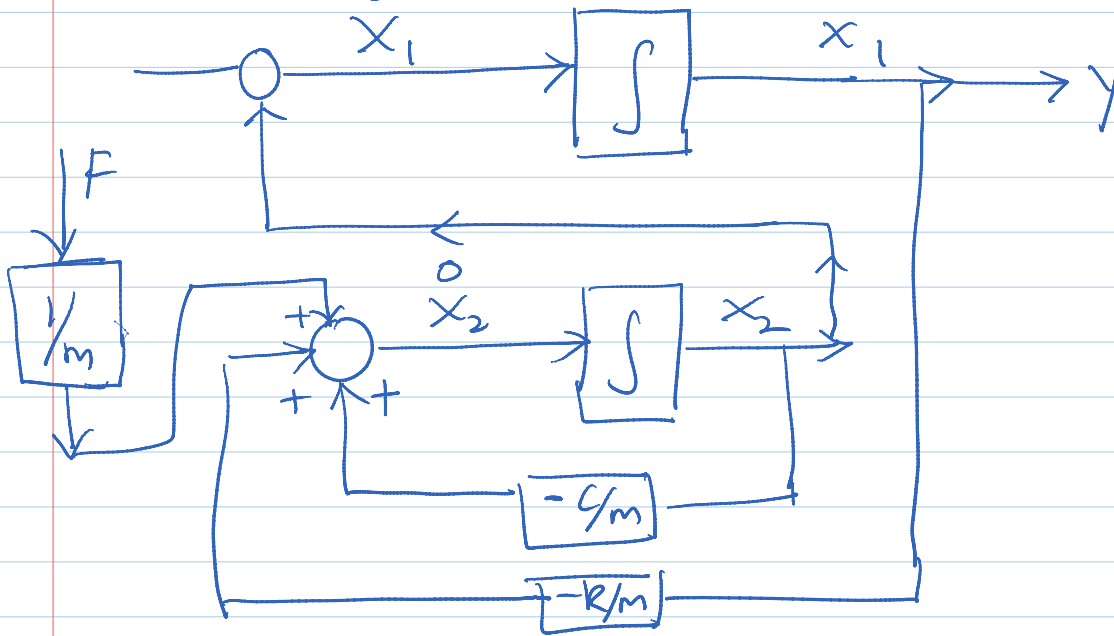

Example 2:

A RLC Circuit

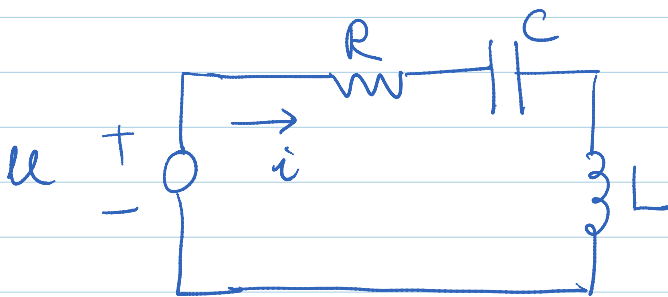

$V_R =$  Voltage drop across resistor  $= iR$

$V_C =$  Voltage drop across capacitor

$$- \quad i = C \frac{dV_C}{dt}$$

$V_L =$  voltage drop across inductor

$$= L \frac{di}{dt}$$

Applying Kirchoffs voltage law

$$V_R + V_C + V_L = u \quad \dots \quad (1)$$

$$V_R = iR; \quad C \frac{dV_C}{dt} = i; \quad V_L = L \frac{di}{dt}$$

lets choose as states

$$x_1 = V_C$$

$$x_2 = i$$

Then we get

$$\dot{x}_1 = \frac{dV_C}{dt} = \frac{i}{C} = \frac{x_2}{C}$$

$$\dot{x}_2 = \frac{di}{dt}$$

From (1) we have

$$iR + V_C + L \frac{di}{dt} = u$$

$$\Rightarrow \frac{di}{dt} = \frac{u}{L} - \frac{V_C}{L} - \frac{iR}{L}$$

$$= \frac{u}{L} - \frac{x_1}{L} - \frac{x_2 R}{L}$$

$$\dot{x}^0 = \begin{bmatrix} \dot{x}_1^0 \\ \dot{x}_2^0 \end{bmatrix} = \begin{bmatrix} 0 & 1/C \\ -1/L & -R/L \end{bmatrix} \begin{bmatrix} x_1 \\ x_2 \end{bmatrix} + \begin{bmatrix} 0 \\ 1/L \end{bmatrix} u$$

$$y = \begin{bmatrix} 0 & R \end{bmatrix} \begin{bmatrix} x_1 \\ x_2 \end{bmatrix}; \quad y \text{ is the voltage} \\ \text{across the resistor}$$

If we had defined

$$x_1 = C V_c$$

$$x_2 = \dot{i}$$

Then we obtain

$$\dot{x}_1^0 = C \frac{dV_c}{dt} = \dot{i} = x_2$$

$$\begin{aligned} \dot{x}_2^0 &= \frac{u}{L} - \frac{V_c}{L} - \frac{V_e}{L} \\ &= \frac{u}{L} - \frac{x_1}{LC} - \frac{R x_2}{L} \end{aligned}$$

and therefore it follows that

$$\begin{pmatrix} \dot{x}_1^0 \\ \dot{x}_2^0 \end{pmatrix} = \begin{bmatrix} 0 & 1 \\ -1/LC & -R/L \end{bmatrix} \begin{bmatrix} x_1 \\ x_2 \end{bmatrix} + \begin{bmatrix} 0 \\ 1/L \end{bmatrix} u$$

$$y = \begin{bmatrix} 0 & R \end{bmatrix} \begin{bmatrix} x_1 \\ x_2 \end{bmatrix}$$

Compare this to the state-space of

Spring-mass-damper system

$$\begin{pmatrix} \dot{x}_1^0 \\ \dot{x}_2^0 \end{pmatrix} = \begin{bmatrix} 0 & 1 \\ -k/m & -c/m \end{bmatrix} \begin{bmatrix} x_1 \\ x_2 \end{bmatrix} + \begin{bmatrix} 0 \\ 1/m \end{bmatrix} F$$

$$\begin{pmatrix} \dot{x}_1 \\ \dot{x}_2 \end{pmatrix} = \begin{bmatrix} 0 & 1 \\ -\frac{k}{m} & -\frac{c}{m} \end{bmatrix} \begin{bmatrix} x_1 \\ x_2 \end{bmatrix} + \begin{bmatrix} 0 \\ \frac{1}{m} \end{bmatrix} F$$

Let's identify

mechanical stiffness  $k = \frac{1}{C}$  where  $C$  is the capacitance

mechanical damping  $c = R$ ;  $R$  is the resistance

mechanical mass  $m = L$ ; the inductance

This provides a mapping between  
Electrical and mechanical systems.

Example: Another choice of state variables.

Note that we have

$$V_R + V_L + V_C = u \quad \text{--- (1)}$$

$$\text{where } V_R = iR$$

$$V_L = L \frac{di}{dt}$$

$$C \frac{dV_C}{dt} = i$$

We can differentiate (1) to obtain

$$R \frac{di}{dt} + L \frac{d^2 i}{dt^2} + \frac{i}{C} = \frac{du}{dt}$$

Looks like a choice for state variables

is

$$x_1 = i; \quad x_2 = \frac{di}{dt}$$

where we obtain

$$\dot{x}_1 = x_2 \quad \text{and}$$

$$\dot{x}_2 = \frac{1}{L} \frac{du}{dt} - \frac{i}{LC} - \frac{R}{L} \frac{di}{dt}$$

$$= \frac{1}{L} \frac{du}{dt} - \frac{x_1}{LC} - \frac{R}{L} x_2$$

Thus,

$$\dot{x} = \begin{bmatrix} \dot{x}_1 \\ \dot{x}_2 \end{bmatrix} = \begin{bmatrix} 0 & 1 \\ -\frac{1}{LC} & -\frac{R}{L} \end{bmatrix} \begin{bmatrix} x_1 \\ x_2 \end{bmatrix} + \begin{bmatrix} 0 \\ \frac{1}{L} \end{bmatrix} \frac{du}{dt}$$
$$y = [1 \ 0] x$$

Here we have  $\frac{du}{dt}$ , not  $u$

The above is not in the form

$$\dot{x} = Ax + Bu$$

Consider the same state space equations with input  $u$  and output  $\tilde{y}$

$$\dot{x} = Ax + Bu$$

$$\tilde{y} = Cx = x_1$$

where  $x_2 = \dot{x}_1$

If the input is  $u$  for the above system  
the output is  $\tilde{y} = x_1$

→ As the system is linear, if the input is changed  
to  $\frac{du}{dt}$  the output will be  $\frac{d\tilde{y}}{dt} = \frac{d}{dt}x_1 = \dot{x}_1 = x_2$

Thus,

$$\dot{x} = Ax + Bu$$

$$y = [0 \ 1] \begin{bmatrix} x_1 \\ x_2 \end{bmatrix} = x_2$$