

Single-phase rectifier circuit

The circuit is represented by a system model implementing the equations:




$$i_D = f(v_D)$$

$$v_D = v_{in} - v_{out}$$

$$i_C = i_D - \frac{v_{out}}{R}$$

$$v_{out} = \frac{1}{C} \int i_C dt$$

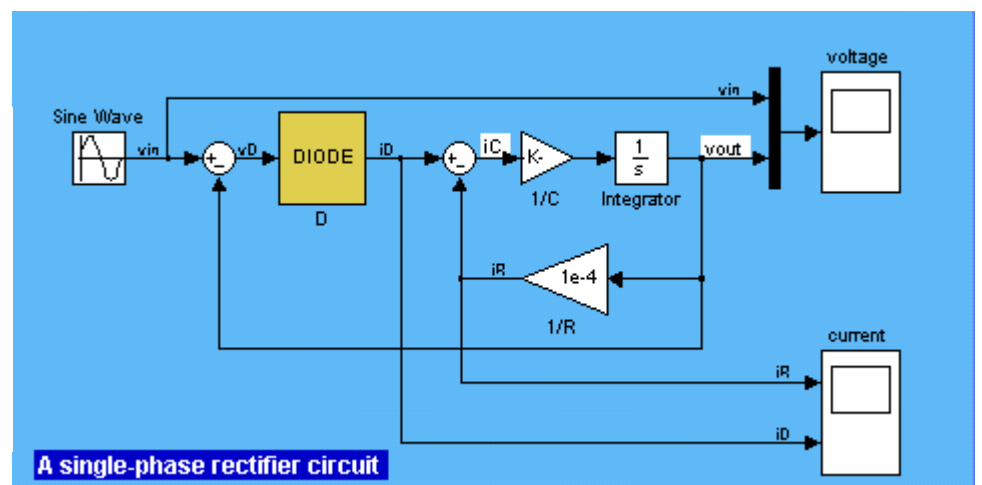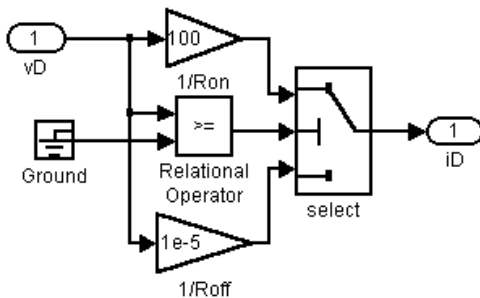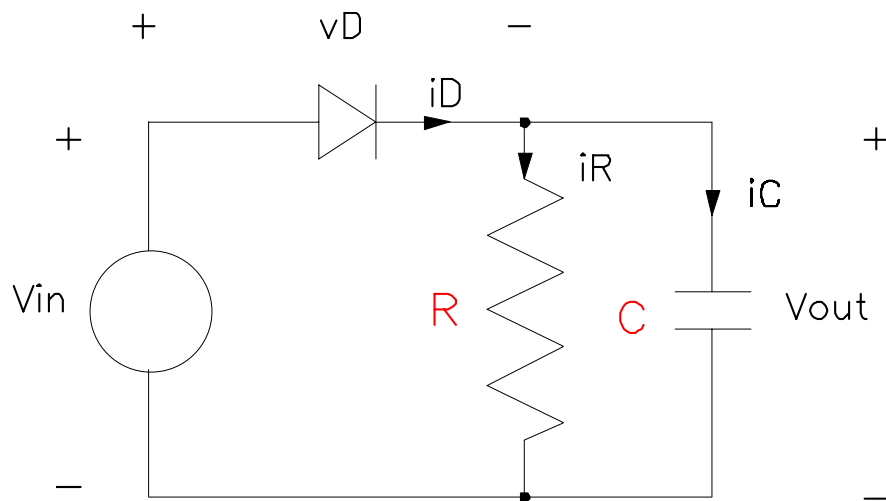The diode is modeled as a piecewise linear resistor whose conductance is large when on ($v_D \geq 0$), and small when off ($v_D < 0$).



Single pulse rectifier

The circuit is represented by a system model which implements the equations:



$$v_D = f(i_D)$$

$$V_L = V_{in} - V_D - V_R$$

$$v_R = Ri$$

$$\mathbf{i} = \frac{1}{L} \int \mathbf{v}_L dt$$

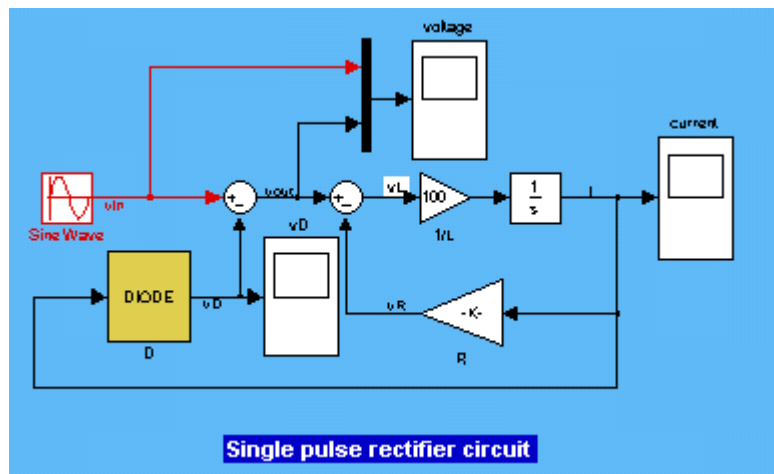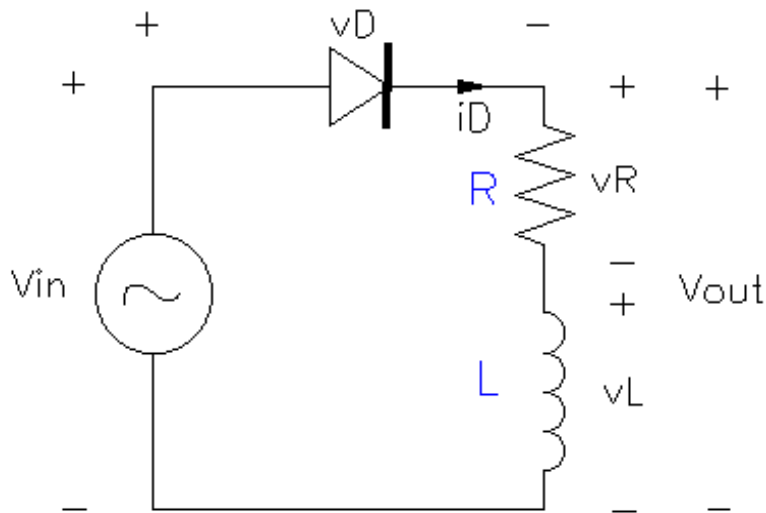The diode is modeled as a piecewise linear resistor whose resistance is small when the diode is on ($i \geq 0$), and large when off ($i < 0$).



Switched RLC circuit

The circuit is closed for a specified time duration "to" when it suddenly opens at the first current zero crossing detected by a logic block defined as subsystem "SWITCH".

